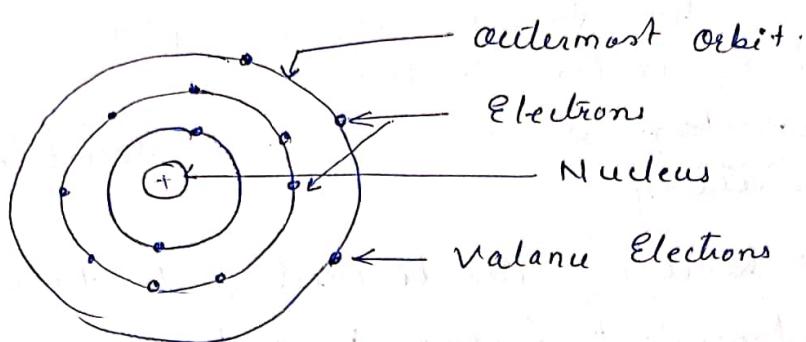


* STRUCTURE OF ATOM



* CONCEPT OF EMF

The Electrical force or pressure that causes the Electrons to move in a particular direction is called as Electromotive force i.e. EMF.

It is also called as voltage or potential difference.
Unit = volts and denoted by V .

* CONCEPT OF CURRENT

Electron current: The current due to flow of Electrons is called Electron current.


Conventional current:

Conventional current is said to be flowing from higher potential to lower potential.

The direction of flow of conventional current is always opposite to that of flow of Electrons or Electron current.

* Potential difference

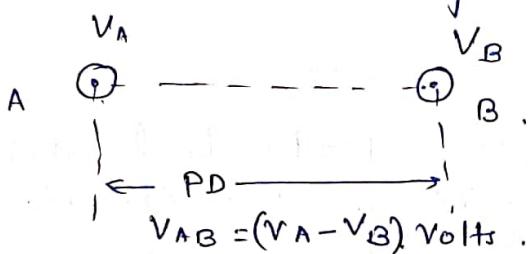Potential difference between any two points is defined as the difference between the electric potentials at those points.



* Power.

It is defined as the product of voltage & current.

$$\text{Power } (P) = V \times I.$$

Unit: Watts.

* Energy.

Electrical Energy is defined as the product of Power and time.

$$\therefore \text{Energy} = \text{Power } (P) \times \text{time } (t).$$

Unit = watts \times seconds or Joules.

Electrical Network

It is interconnection of various active & Passive Elements

Active Source

The source which gives out energy is called as active source.

Eg: Voltage source, current source, generator, Battery

Active sources are divided into two types.

- ① Independent / uncontrolled source.
- ② Dependent / controlled source.

① Independent / uncontrolled source

The source whose magnitude is not dependent or cannot be controlled by any other parameter of given network then it is called as independent or uncontrolled source.

They are classified as.

- I Independent voltage source. (symbol)
- II Independent current source. (symbol)

① Independent voltage source.

① Ideal voltage source


Ideal voltage source is that source whose terminal voltage remains constant irrespective of change in current flowing through it.

The source resistance of an ideal voltage source is zero. [Therefore terminal voltage remains constant without load or with load]

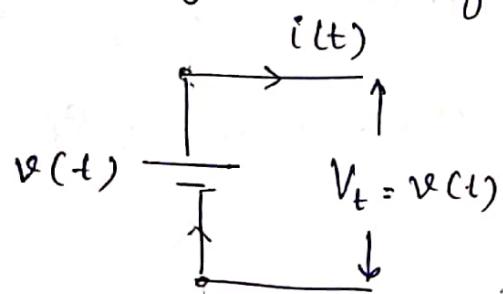(b) Practical voltage source

In practice the ideal voltage source discussed earlier does not exist.


The practical voltage source has some internal resistance, due to which terminal voltage across it goes on decreasing for increasing value of current coming out of it.



Ideal voltage source.

$$V_t' = V(t)$$


$$R_s = 0$$

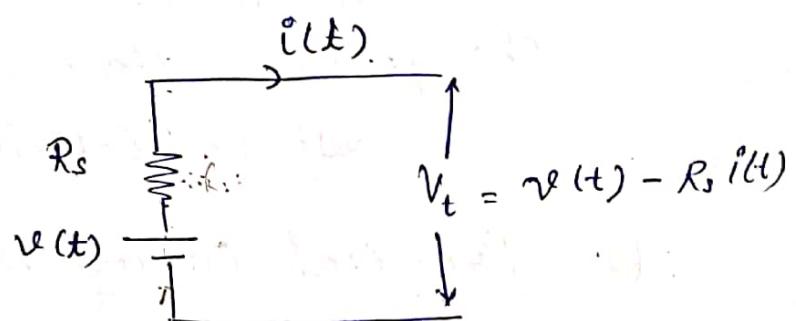

Practical voltage source

$$V_t = V(t) - R_s i(t).$$

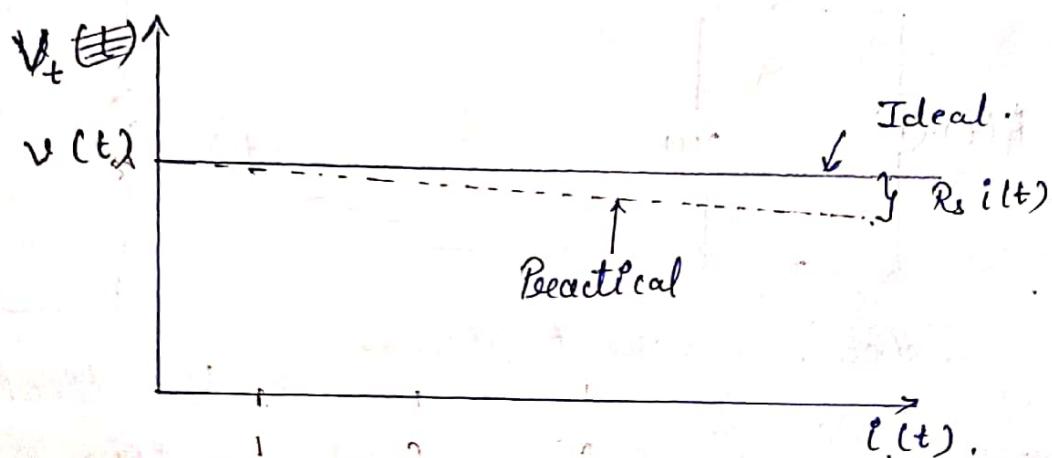Characteristics of Ideal and Practical voltage Source



II

Independent current sources

They are further classified as:

- (a) Ideal current source.
- (b) Practical current source.



(a) Ideal current source

Ideal current source is that source whose terminal current remains constant irrespective of any change in voltage across it.

It has infinite internal resistance ($R_i = \infty$).

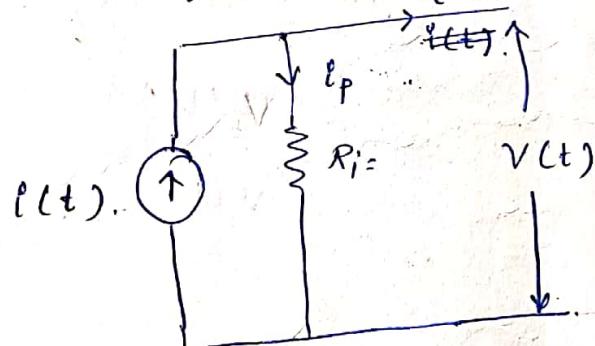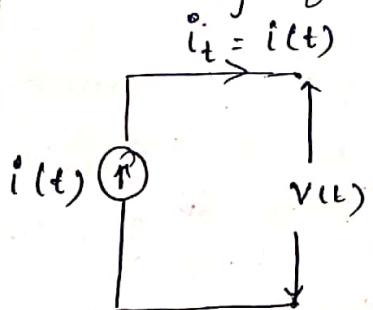(b) Practical current source

The Practical current source has will have a finite shunt resistance (internal). which is assumed to be parallel with source. Because of this resistance, the output current goes on decreasing for increasing value of voltage across it.



Ideal current source

$$R_i = \infty$$


$$i_t = i(t)$$

Practical current source

$$i(t) = i_t + i_p$$

$$i_t = i(t) - i_p$$

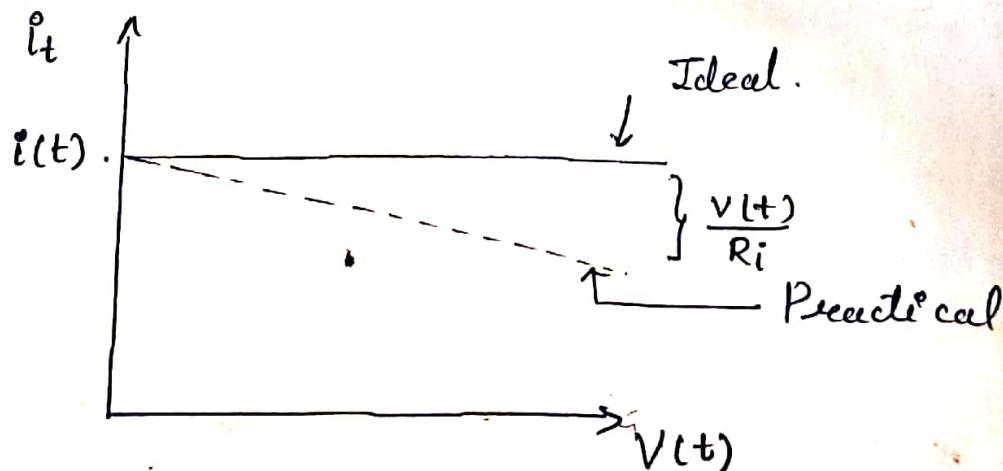Characteristics of Ideal & Practical current source




② Dependent or Controlled source


The source whose Magnitude is depend upon or can be controlled by any other parameter of the given Network.

They are classified as.

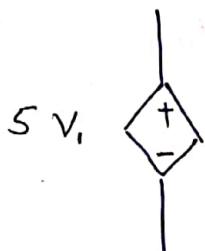
- 1] Voltage Controlled voltage source. (V_{CVS})
- 2] Voltage Controlled current source (V_{CCS})
- 3] Current Controlled current source ($CCCS$)
- 4] Current Controlled voltage source ($CCVS$)




V_{CVS}

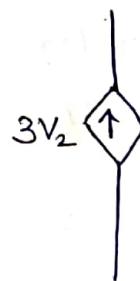

V_{CCS}

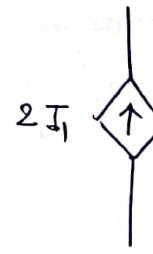

$CCCS$

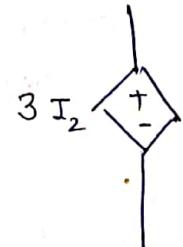

$CCVS$

Passive Elements.

The Elements which consumes Energy is called as Passive Element.

i) Resistor (R)

Resistance of a material is defined as the opposition to flow of current. It is measured in Ohms (Ω). The symbol is R .

$$R = \rho \frac{l}{a}$$

$R \rightarrow$ Resistance. (Ω)

$\rho \rightarrow$ Resistivity of the material. ($\Omega \cdot m$)

$l \rightarrow$ length of the conductor. (m)

$a =$ Cross section area. (m^2)

iv #

Inductance (L)

Inductance is defined as the property of the coil by which an EMF is induced when the current passing through it changes with respect to time.

$$V_L(t) \propto \frac{di}{dt} i(t).$$

$$V_L(t) = L \frac{di}{dt} i(t) \rightarrow \text{Voltage across Inductor.}$$

current through inductor

Integrated w.r.t 't'

$$\int V_L(t) dt = L i_L(t).$$

$$i_L(t) = \frac{1}{L} \int V_L(t) dt.$$

The unit of Inductance is ~~Henry~~ Henry (H).

iii) #

Capacitance (C)

A Capacitance is defined as the property of a device by which it carries current when its voltage is changed with respect to time.

Or.

Charge developed between plates of capacitor is directly proportional to the potential difference between the plates; the constant of proportionality is called Capacitance.

$$Q = CV_c$$

Differentiate w.r.t t

$$\frac{dQ}{dt} = C \frac{dV_c}{dt}$$

current through capacitance.

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

Integrate w.r.t. time.


$$\int i_c(t) \cdot dt = C \times V_c(t).$$

$$V_c(t) = \frac{1}{C} \int i_c(t) \cdot dt \rightarrow \text{Voltage across Capacitor.}$$

The unit of Capacitance is farad.

I Resistances in series.

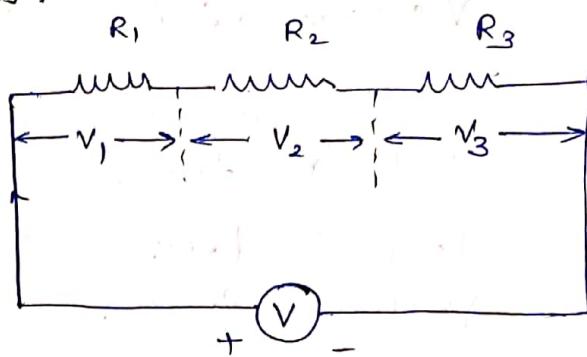Consider three resistances R_1, R_2, R_3 are connected in series across a voltage source 'V' volts.



In series circuit current through all resistances is same but the voltage across each resistance is different.

$$\text{Let } V_1 \rightarrow \text{voltage across } R_1 = IR_1$$

$$V_2 \rightarrow \text{voltage across } R_2 = IR_2$$

$$V_3 \rightarrow \text{voltage across } R_3 = IR_3$$

The applied voltage 'V' is algebraic sum of voltage across each element.

$$V = V_1 + V_2 + V_3$$

$$= IR_1 + IR_2 + IR_3$$

$$= I(R_1 + R_2 + R_3)$$

$$\text{But } V = IR_T$$

$$\therefore R_T = R_1 + R_2 + R_3$$

$$R_T = R_1 + R_2 + R_3$$

where R_T is Total or Equivalent resistance when "n" no. of resistances are connected in series, Total Resistance is given by.

$$R_T = R_1 + R_2 + R_3 + \dots + R_n$$

Voltage division Rule.

In series combination current flowing in each resistance is same but voltage is divided. To calculate individual voltage, we use Voltage division Rule,


$$V_1 = \left(\frac{R_1}{R_1 + R_2 + R_3} \right) \times V$$

$$V_2 = \left(\frac{R_2}{R_1 + R_2 + R_3} \right) \times V$$

$$V_3 = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) \times V$$

Resistances in Parallel

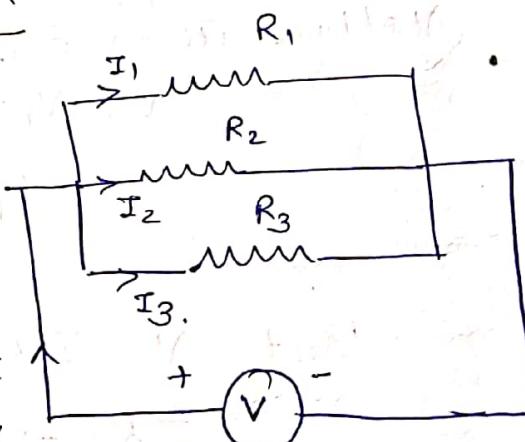The resistances are said to be connected in parallel when one end of each resistance is connected to one common point & remaining end of each resistance is connected to another common point.



Consider the three resistances R_1, R_2, R_3 are connected in parallel across a source voltage 'V' volts. The voltage across each resistance is same but current is divided given by

~~I = V~~ Total current,

$$\therefore I = I_1 + I_2 + I_3$$

Also

$$I_1 = \frac{V}{R_1}; \quad I_2 = \frac{V}{R_2}; \quad I_3 = \frac{V}{R_3}$$

$$\text{But } I = \frac{V}{R_T}$$

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\Rightarrow \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

- When n no. of Resistances are connected in parallel, then the Equivalent resistance is given by

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$


Current Division Rule

In parallel connection, voltage across each resistance is same but current divides. And to calculate current through each branch can be done by using Current division Rule.

for Two Resistance in Parallel

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) \times I$$
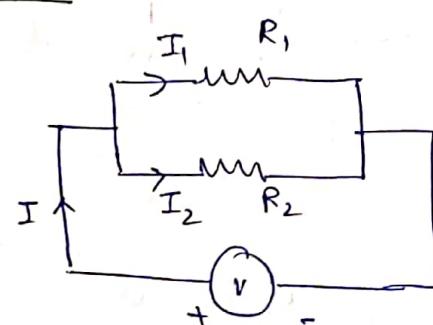
$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) \times I$$




When Three Resistances are in parallel.

$$I_1 = \left(\frac{R_2 \cdot R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right) \times I$$


$$I_2 = \left(\frac{R_1 \cdot R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1} \right) \times I$$
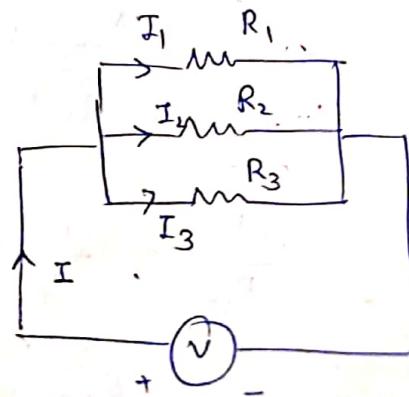
$$I_3 = \left(\frac{R_1 \cdot R_2}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right) \times I$$



Numericals on series, parallel and ohm's law

T.S.-1.

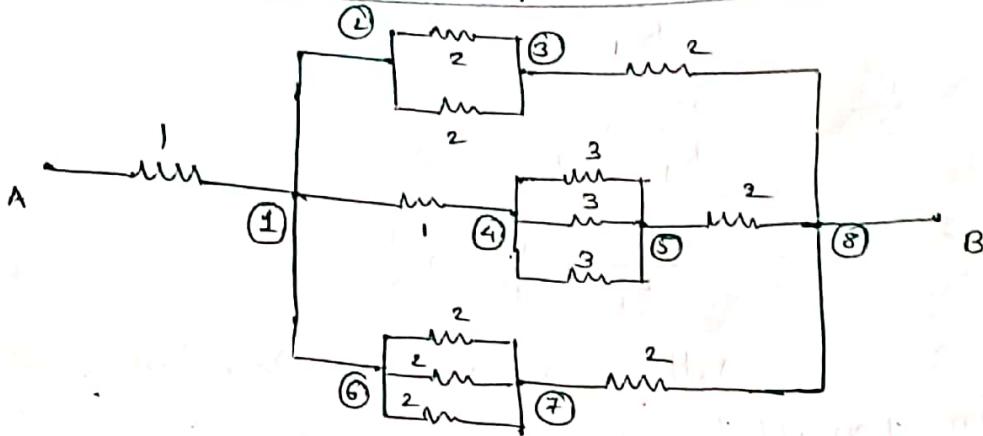

Calculate R_{AB} .



$$\frac{1}{R_{23}} = \frac{1}{2} + \frac{1}{2}; \quad \frac{1}{R_{45}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3}$$


$$R_{23} = 1\ \Omega$$

$$\frac{1}{R_{45}} = \frac{3}{3}$$


$$R_{45} = 1\ \Omega$$

$$\frac{1}{R_{67}} = \frac{1}{2} + \frac{1}{2} + \frac{1}{2} = \frac{3}{2}$$

$$R_{67} = 0.66\ \Omega$$

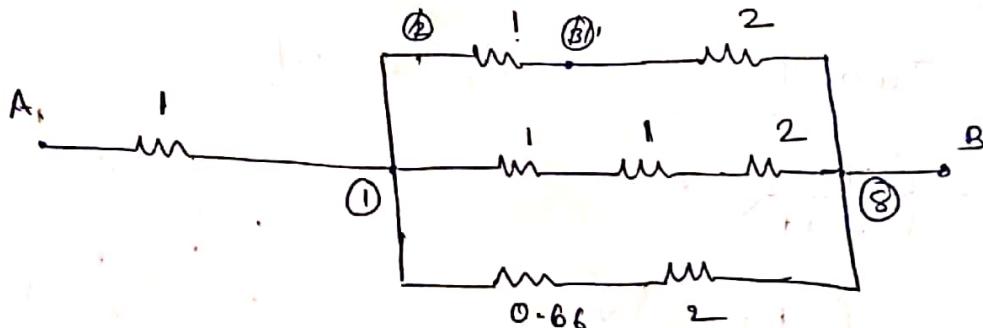

Redraw.

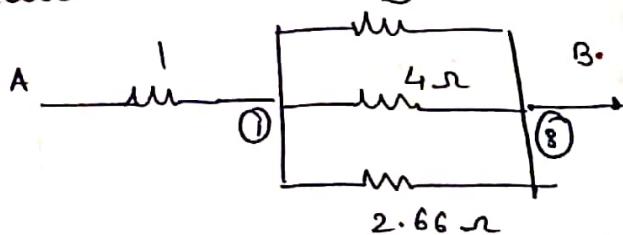

$$\frac{1}{R_{18}} = \frac{1}{3} + \frac{1}{4} + \frac{1}{2.66} = 1.04\ \Omega$$

$$R_{AB} = 1 + 1.04 = 2.04\ \Omega$$

1 & 2 in series

$$R'_{18} = 1+2=3\ \Omega$$

1 & 1 & 2 in series

$$R''_{18} = 1+1+2=4\ \Omega$$



0.66 & 2 in series

$$R'''_{18} = 2.66\ \Omega$$

Calculate Equivalent Resistance Across AB.

Soln →

Redraw.

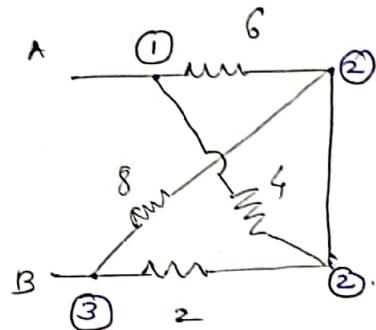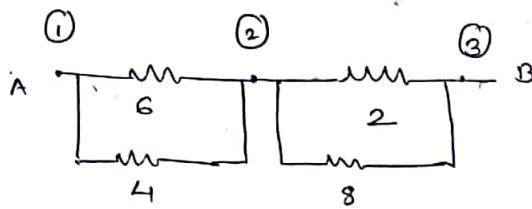


⇒ 6 & 4 are in parallel.

$$\frac{1}{R_{12}} = \frac{1}{6} + \frac{1}{4} = [2.4 \Omega, = R_{12}]$$

⇒ 8 & 2 are in parallel.

$$\frac{1}{R_{23}} = \frac{1}{8} + \frac{1}{2} = \frac{10}{16}$$



$$R_{23} = 1.6 \Omega$$

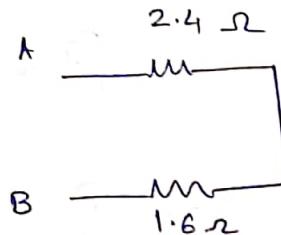

Now, 2.4 Ω & 1.6 Ω are in series

$$\therefore R_{AB} = 2.4 + 1.6 = 4 \Omega$$

Calculate I

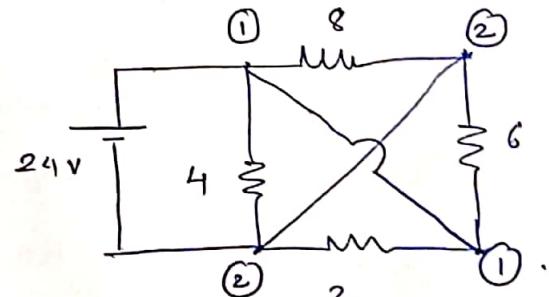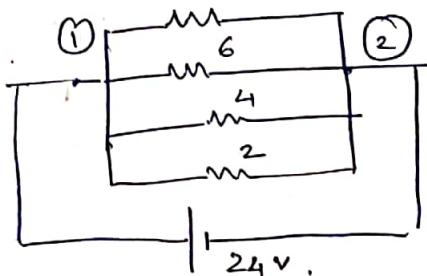

All Resistances are in parallel.


$$\begin{aligned} \frac{1}{R_{12}} &= \frac{1}{8} + \frac{1}{6} + \frac{1}{4} + \frac{1}{2} \\ &= \frac{6+12+8+24}{48} = \frac{50}{48} \end{aligned}$$

$$R_{12} = 0.96 \Omega$$


$$I = \frac{24}{0.96} = 25 \text{ Amp.}$$

Calculate R_{AB} .

*

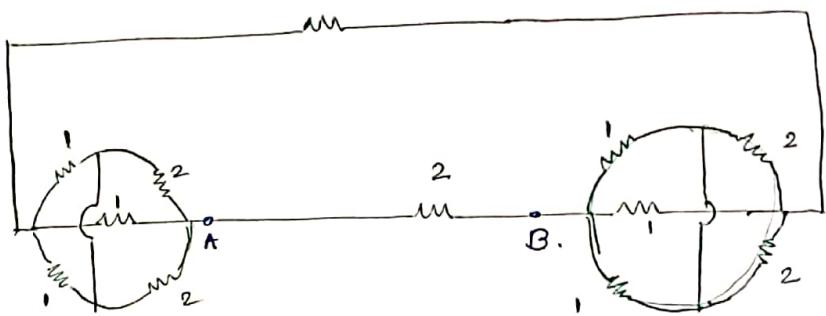

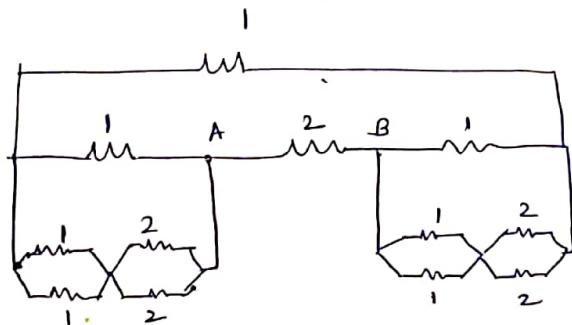\Rightarrow Circuit can be simplified as follows.



1 & 1 are in parallel

$$R_{1||1} = \frac{1 \times 1}{1+1} = 0.5$$

2 & 2 are in parallel

$$R_{2||2} = \frac{2 \times 2}{2+2} = 1 \Omega$$

Then 1 & 0.5 are in series.

$$R = 1 + 0.5 = 1.5 \Omega$$




Now, 1 & 1.5 are in Parallel.

$$R_{1||1.5} = \frac{1.5 \times 1}{1+1.5} = \frac{1.5}{2.5} = 0.6 \Omega$$

\Rightarrow Now, 0.6, 0.6 & 1 are in series.
 $= 0.6 + 0.6 + 1 = 2.2 \Omega$.


Now 2.2 is in parallel 2.
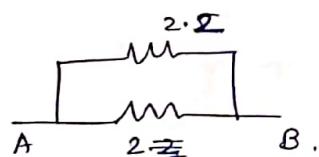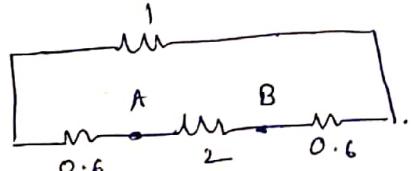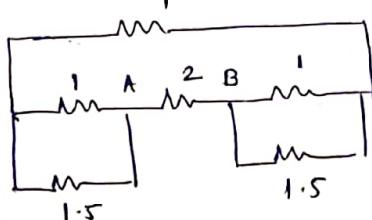
$$R_{AB} = \frac{2.2 \times 2}{2+2.2} = 1.047 \Omega$$




N-17
Q.

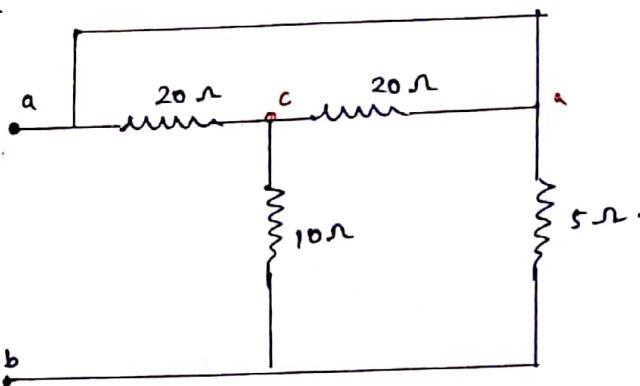
Find R_{eq} between the terminals a-b for the circuit




⇒.

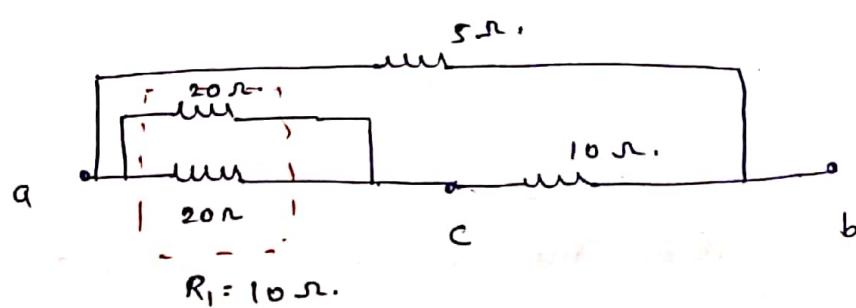
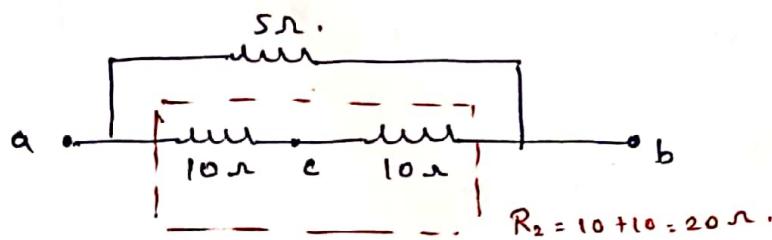
$$R_1 = 20 \parallel 20 = \frac{20 \times 20}{20 + 20} = 10 \Omega.$$



Redraw.

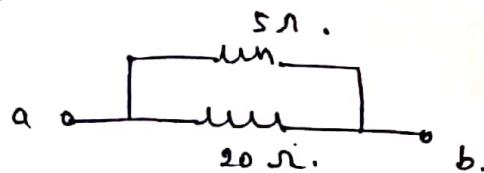


$$R_{ab} = 20 \parallel 5 = \frac{20 \times 5}{20 + 5} = \frac{100}{25}$$

$$\boxed{R_{ab} = 4 \Omega.}$$

Calculate Equivalent Resistance between terminals A & B ?

Q. $R_{AB} = ?$

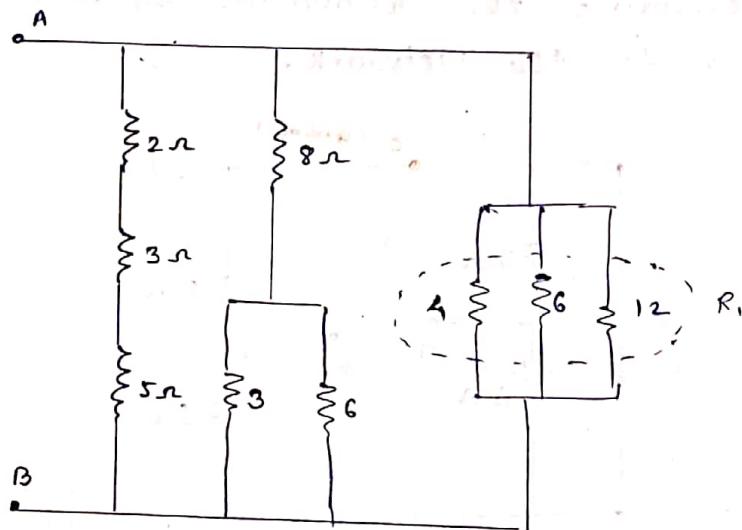

$\Rightarrow 2\Omega, 3\Omega \text{ & } 5\Omega$ are in series


$\therefore 3\Omega$ is in parallel with 6Ω .

$$3 \parallel 6 = \frac{3 \times 6}{3+6} = 2\Omega$$

$4\Omega, 6\Omega \text{ & } 12\Omega$ are in parallel.


$$4 \parallel 6 \parallel 12 = \frac{1}{R_1} = \frac{1}{4} + \frac{1}{6} + \frac{1}{12}$$

$$R_1 = 2\Omega$$

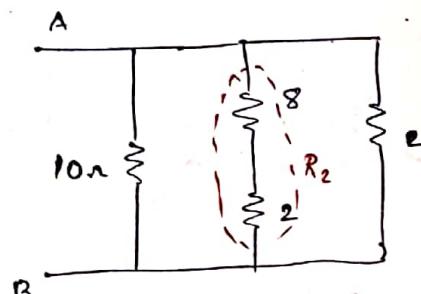

8Ω & 2Ω are in series

$$R_2 = 8 + 2 = 10\Omega$$

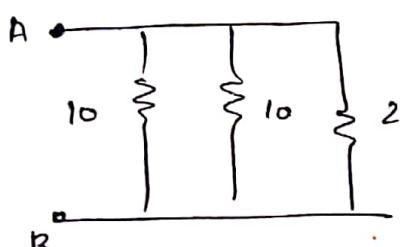



$$10 \parallel 10 \parallel 2$$

$$\frac{1}{R_{AB}} = \frac{1}{10} + \frac{1}{10} + \frac{1}{2}$$

$$R_{AB} = \frac{10}{7}\Omega = 1.4285\Omega$$


Q.

Determine the resistance between the terminals a-b in the network.

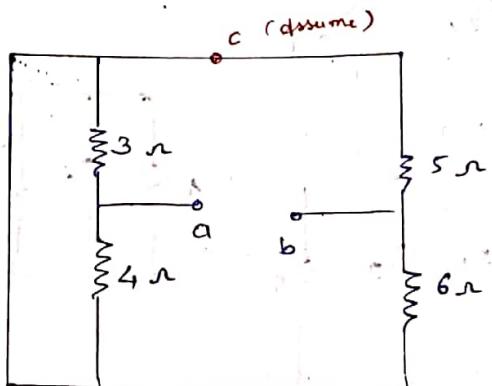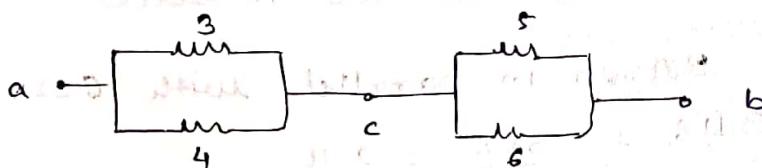 \Rightarrow 

$$R_{ac} = \frac{3 \parallel 4}{3+4} = \frac{3 \times 4}{7} = \frac{12}{7} \Omega$$
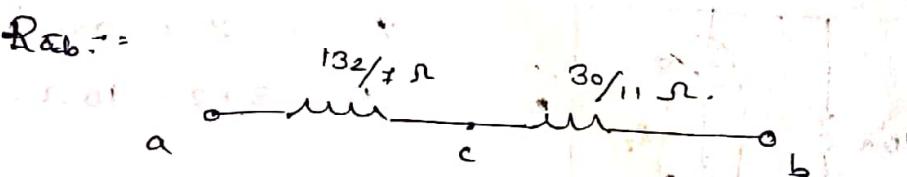
$$R_{bc} = \frac{5 \parallel 6}{5+6} = \frac{5 \times 6}{11} = \frac{30}{11} \Omega$$




$$R_{ab} = \frac{12}{7} + \frac{30}{11} = 4.44 \Omega$$

Total $\rightarrow 4.44 \Omega$

Imp:


Q. find the current I for given network.

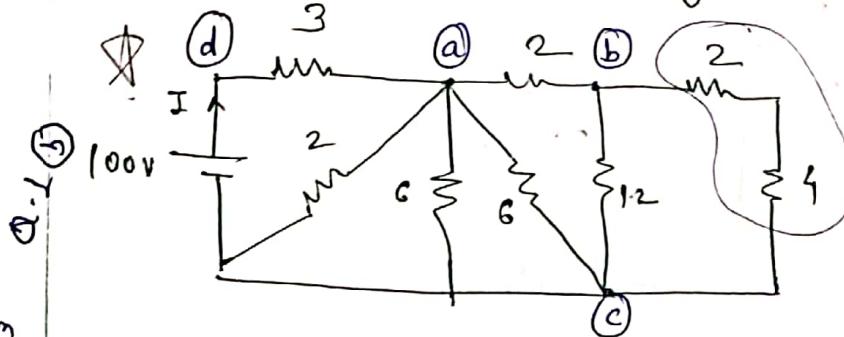

Soln

2 & 4 are in series in parallel with 12
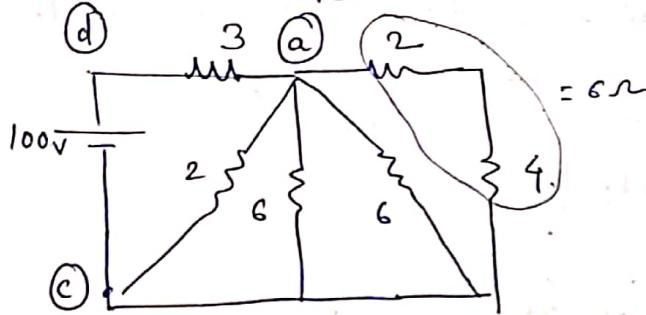
$$\frac{1}{R_{bc}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{bc} = 4 \Omega$$




$$\frac{1}{R_{ac}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{6} + \frac{1}{2}$$

$$\frac{1}{R_{ac}} = \frac{1}{2} + \frac{1}{2} = 1$$

$$R_{ac} = 1 \Omega$$

Redraw

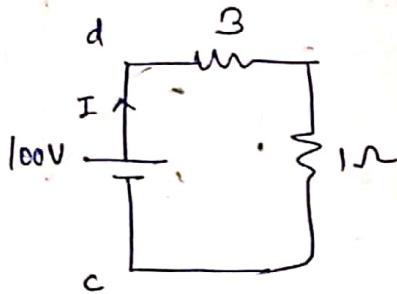

$$\Rightarrow R_{dc} = 4 \Omega$$


$$I = \frac{100}{4}$$

$$I = 25 \text{ Amps}$$


Removal of Redundant Branches

A redundant branch (or group of branches) is the one which can be removed from the circuit without affecting the circuit.

CASE I : Any branch that does not carry current is redundant and hence can be removed.

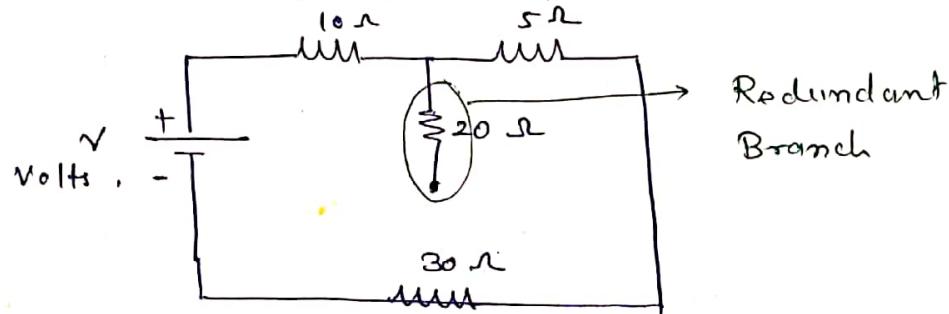

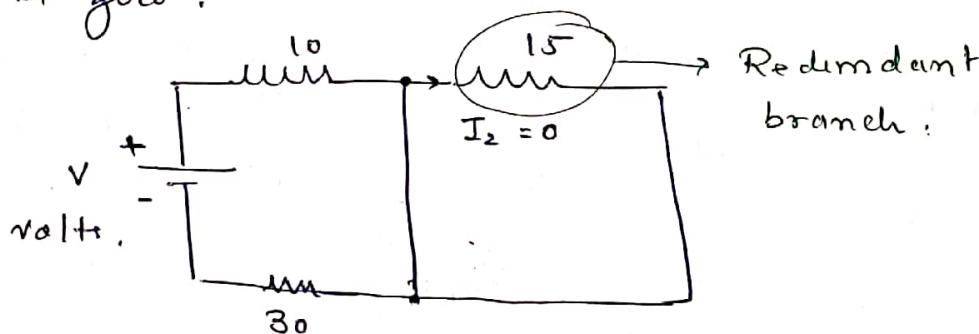CASE II : Any branch which has both terminals short circuited will also be a redundant branch because current flowing through such branch will be zero.




Source Transformation

$$V = IR$$

$$I = \frac{V}{R}$$

25


From voltage source, to current source.

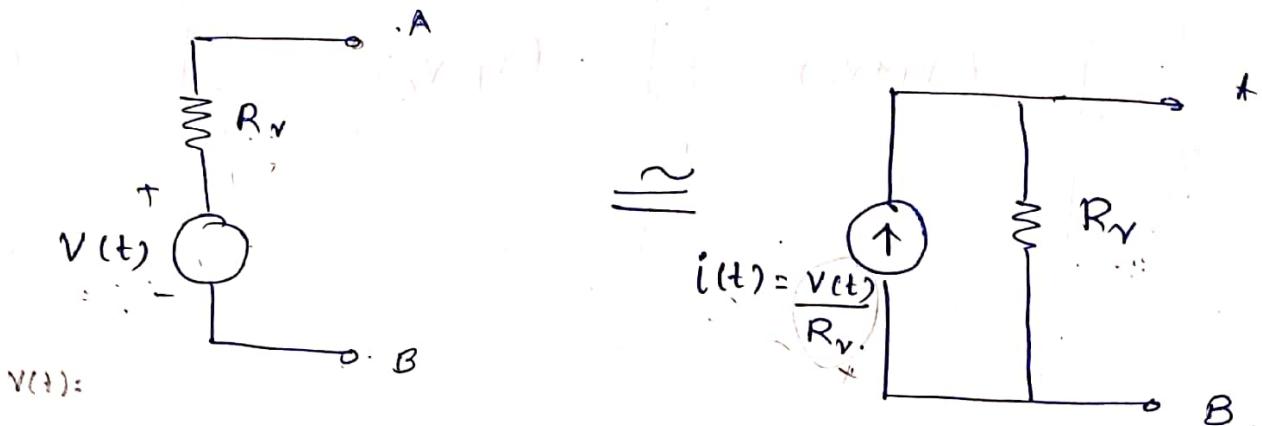

Voltage Source

Equivalent Current Source.



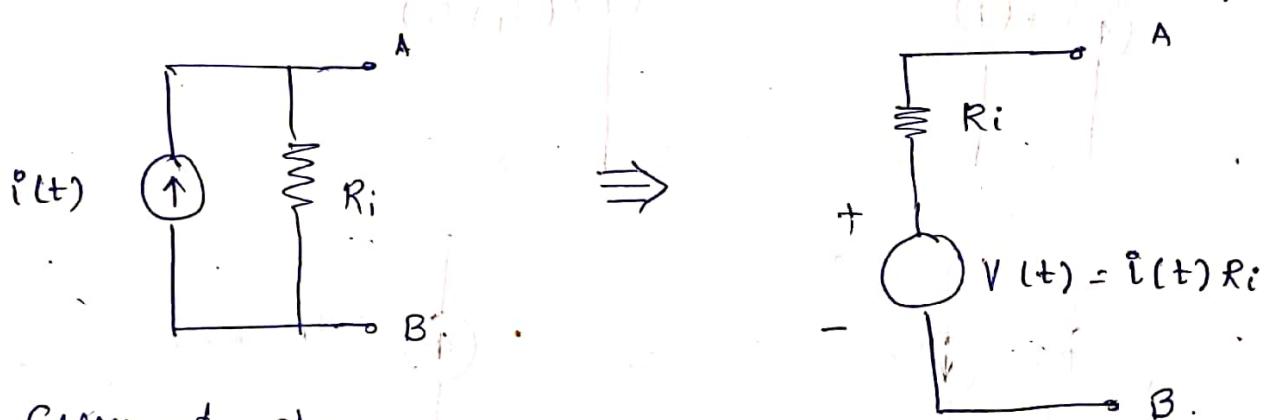
From known current source to voltage source.








Current Source

Equivalent Voltage Source

Voltage Sources in Series

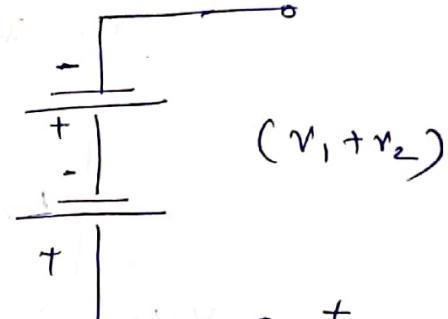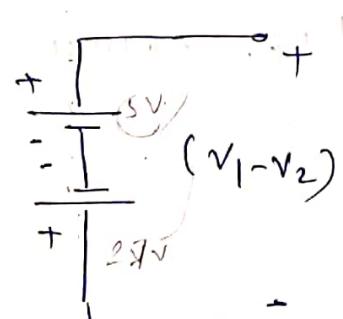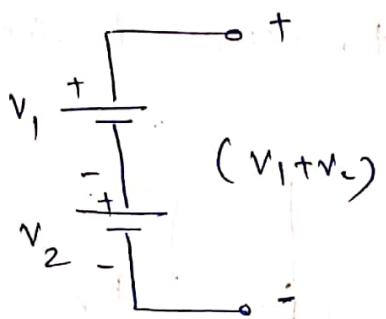

Current Sources in Parallel

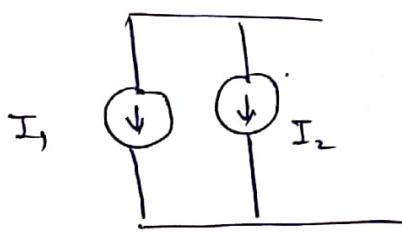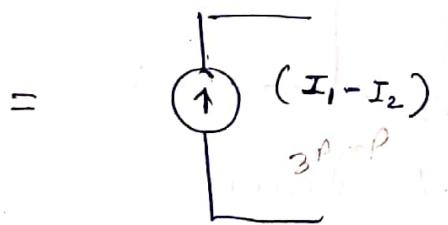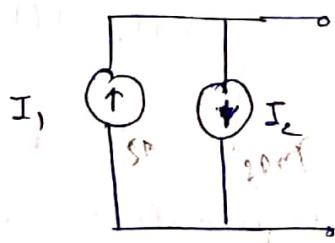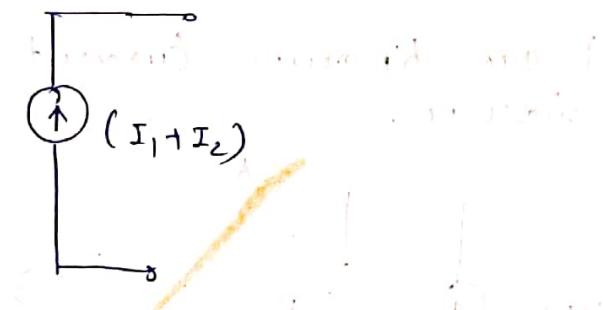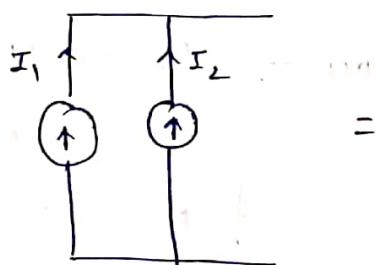

Note :


- 1) No two ideal current source of different magnitude are connected in series.
- 2) Ideal voltage source of different magnitude are never connected in parallel.

Various combinations of sources.


$$V = IR$$

$$I = \frac{V}{R}$$

- ① Equivalent voltage source in series.

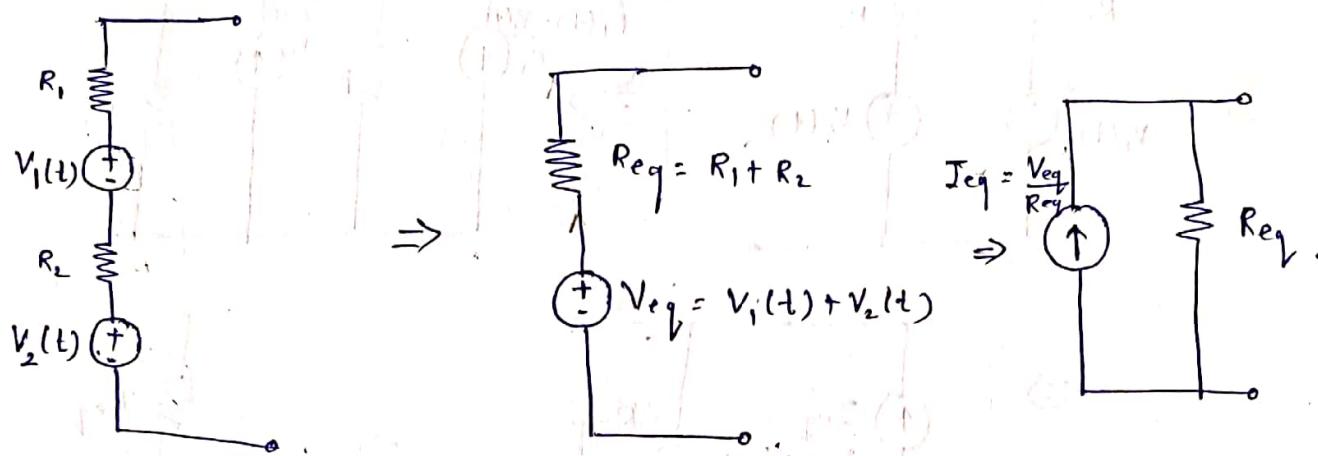

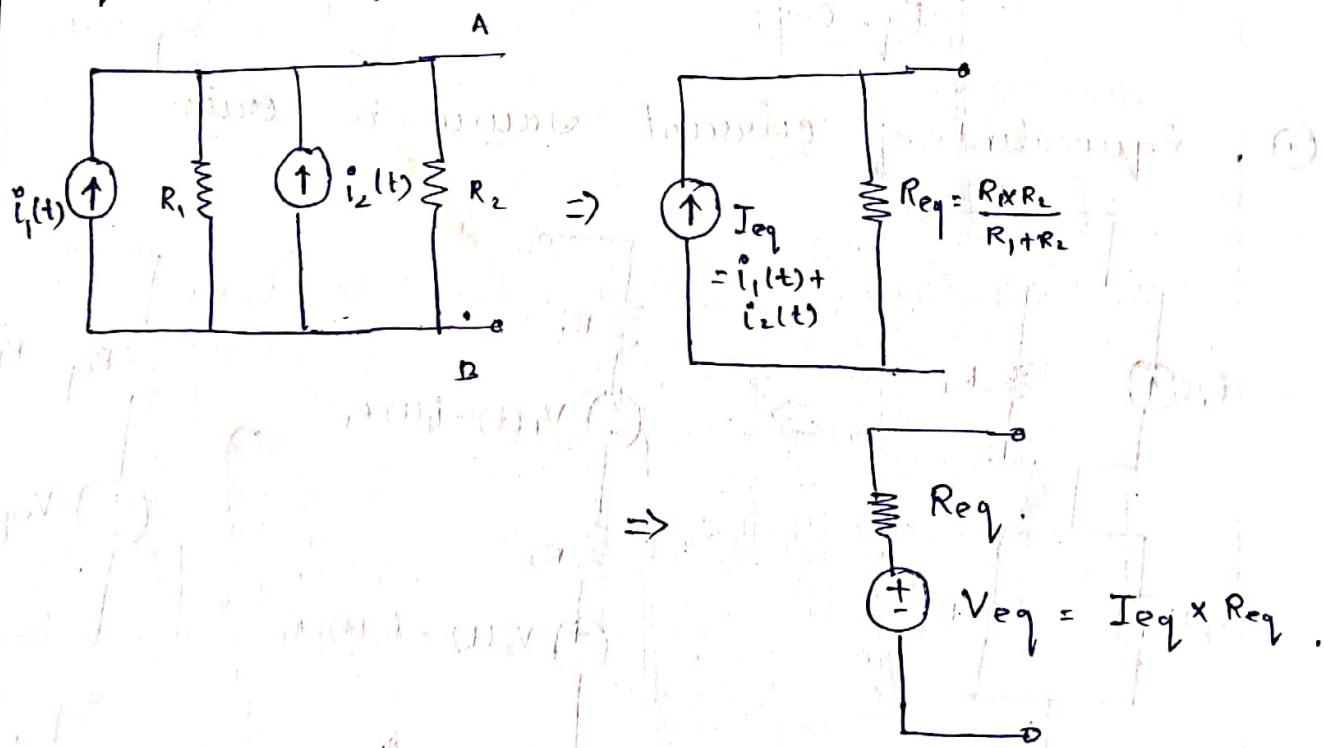
- ② Equivalent of current source in parallel.




28

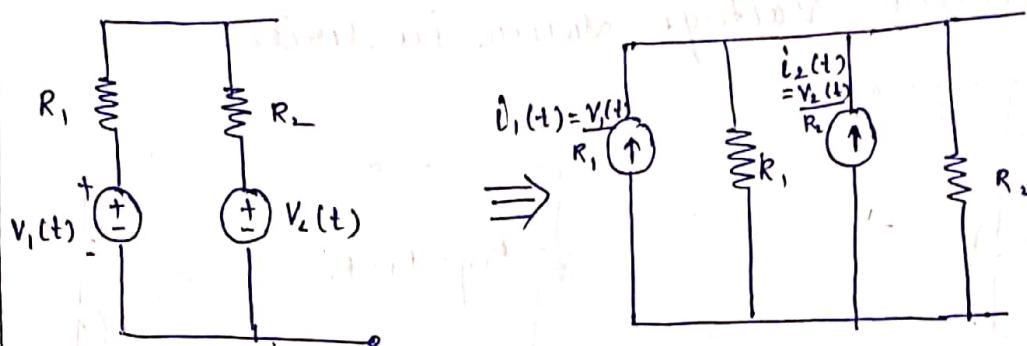(3)

Equivalent of voltage source in parallel.



$$i_1(t) = \frac{V_1(t)}{R_1}$$

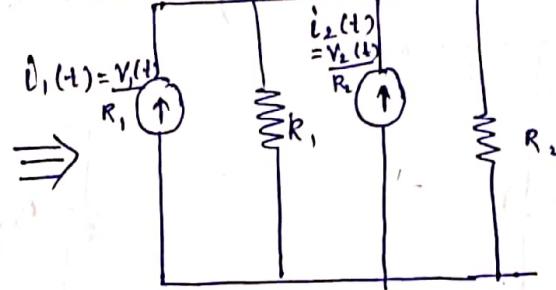


$$\Rightarrow \begin{array}{l} I_{eq} = i_1(t) + i_2(t) \\ R_{eq} = \frac{R_1 R_L}{R_1 + R_L} \end{array}$$

Eq. C.S.

$$\Rightarrow \begin{array}{l} R_{eq} \\ V_{eq} = I_{eq} \cdot R_{eq} \end{array}$$

Eq. V.S.

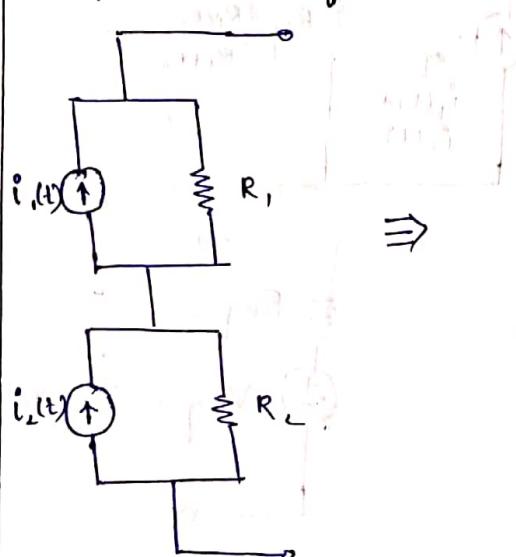(4) Equivalent of current source in series



$$\Rightarrow \begin{array}{l} V_1(t) = i_1(t) R_1 \\ V_2(t) = i_2(t) R_2 \end{array}$$




$$\Rightarrow \begin{array}{l} R_{eq} = R_1 + R_2 \\ V_{eq} = V_1(t) + V_2(t) \end{array}$$

Eq. V.S.


$$\Rightarrow \begin{array}{l} V_{eq} \\ \frac{V_{eq}}{R_{eq}} = I_{eq} \end{array}$$

⑤

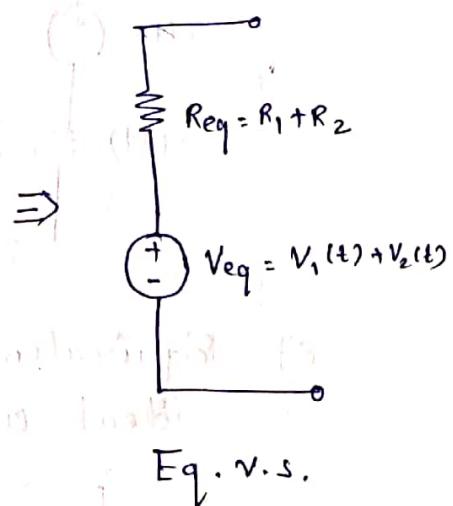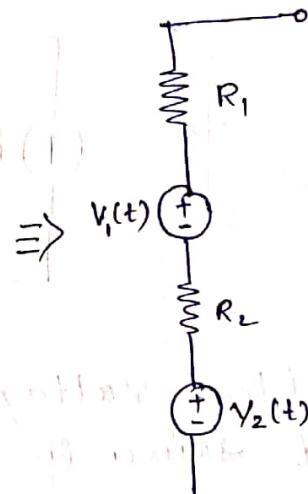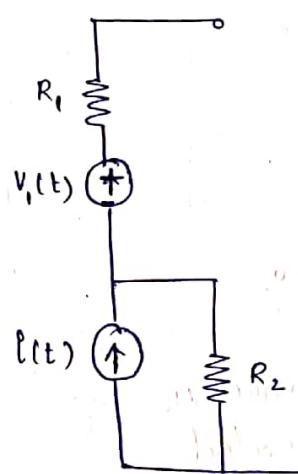Equivalent of voltage source & current source in series.






Eq. v.s.

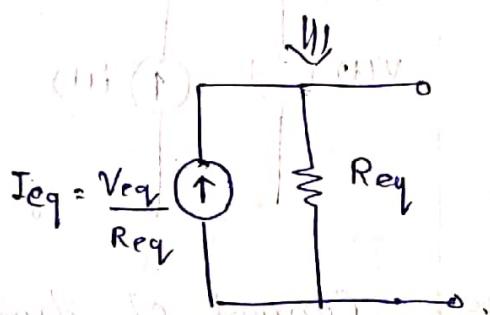


⑥

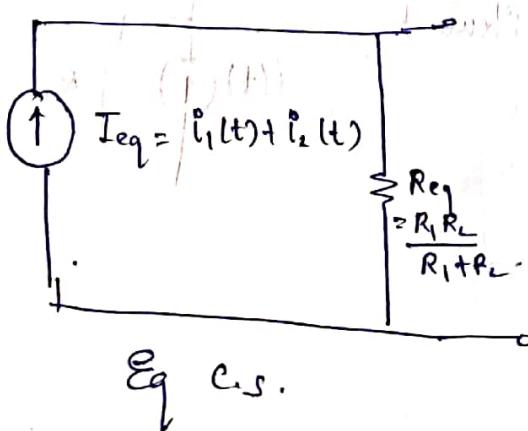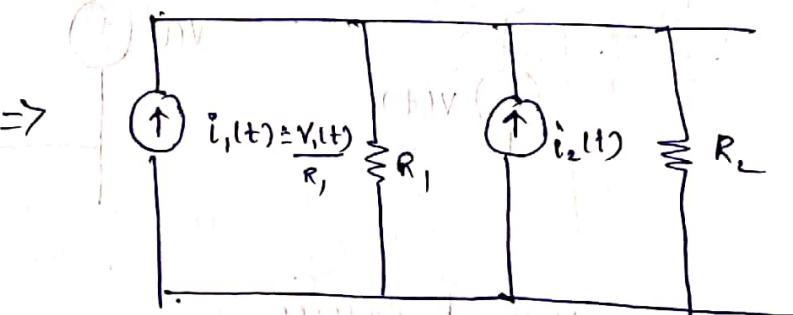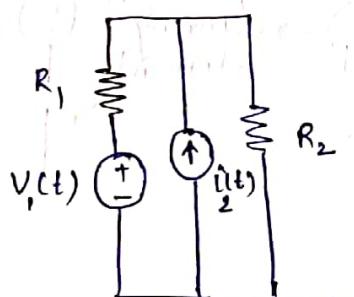Equivalent of voltage source & current source in parallel.





Eq. c.s.

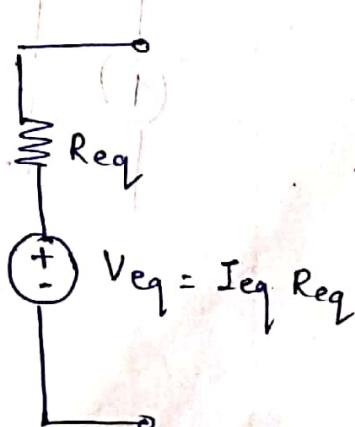

30



7).

Equivalent of Ideal voltage source and ideal current source in series.

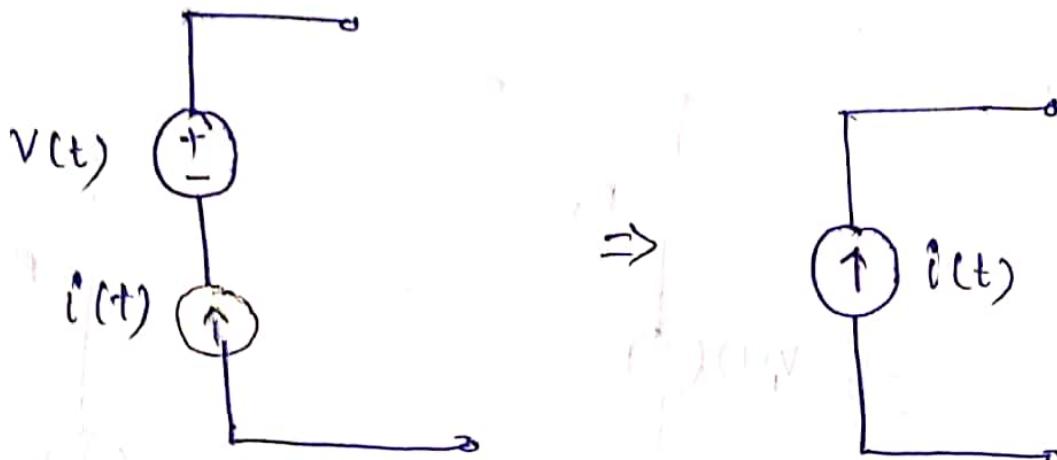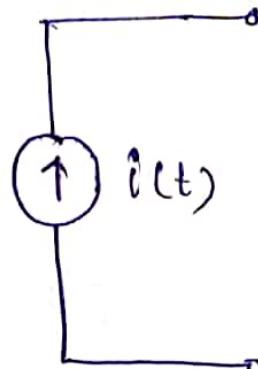 \Rightarrow 



8)

Equivalent of ideal voltage source
ideal current source in parallel

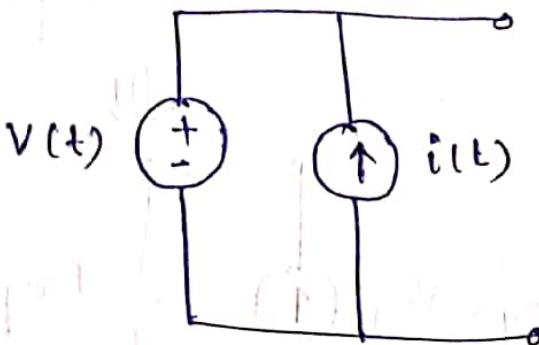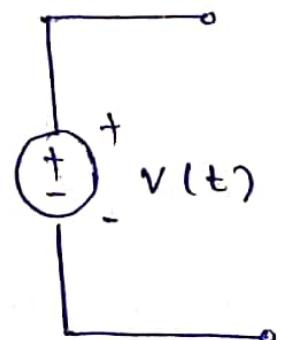 \Rightarrow 

Numerical :



(1)

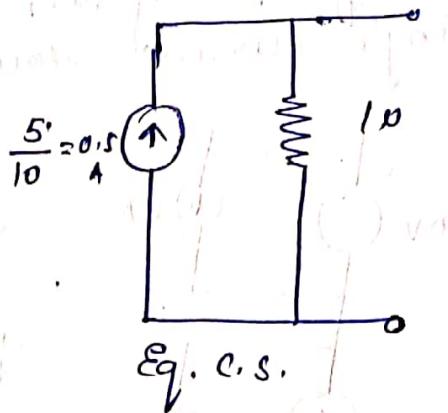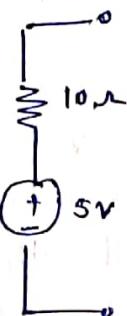

Eq. C.S.




Transform into
current source = ?

(2). Transform into voltage source

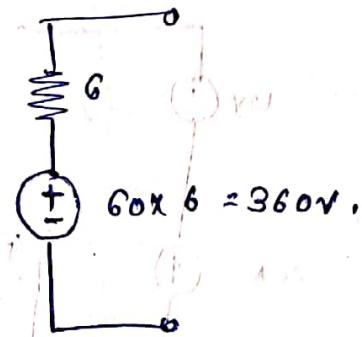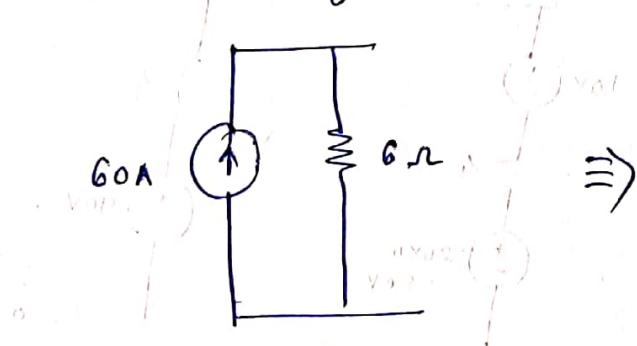


③ convert the Network into a single voltage source.

*

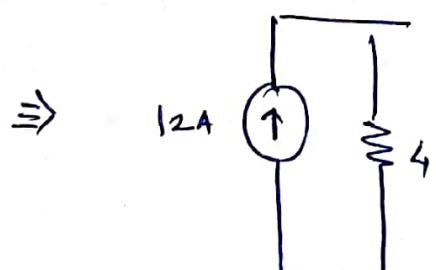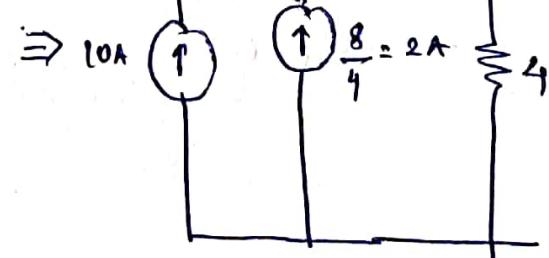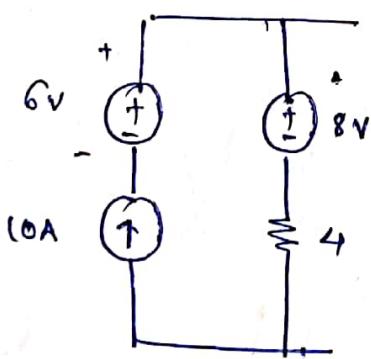


Eq. C.S.

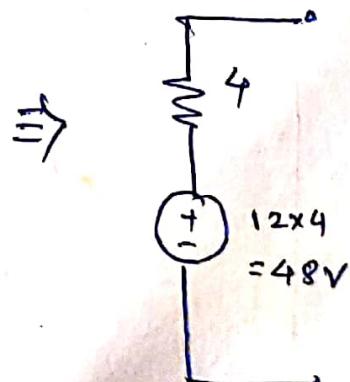


(4)

Transform a given Network into a single current source.


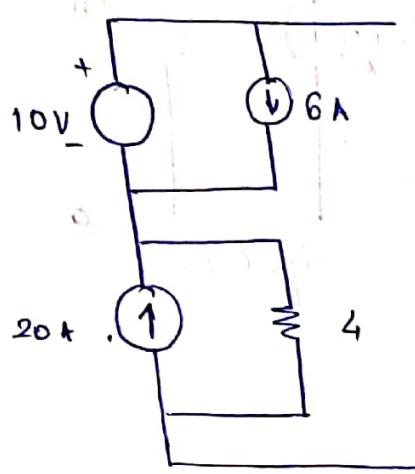


Ideal V.S. of 10V

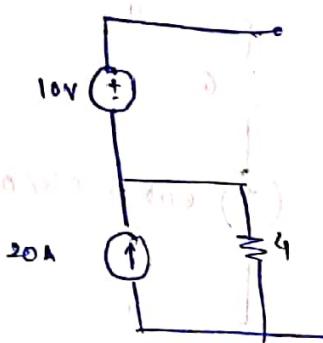
& Ideal C.S. of 6A are connected only in parallel therefore V.S. of 10V will remain in the circuit only.



Convert C.S. into V.S.

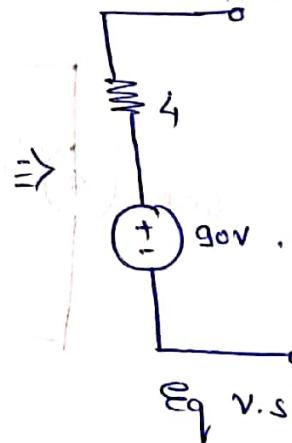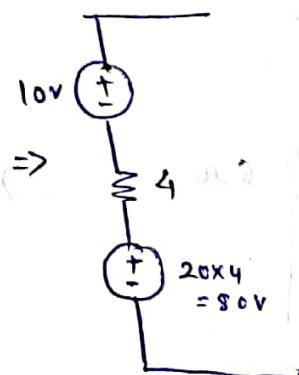


Eq. V.S.

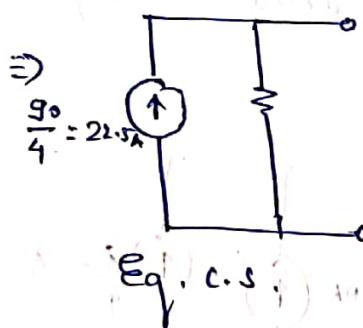


Eq. C.S.

Transform given Network into a equivalent


Current source.

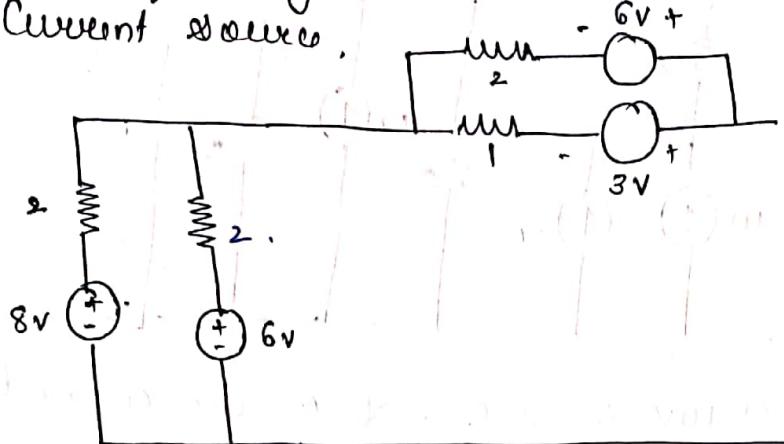

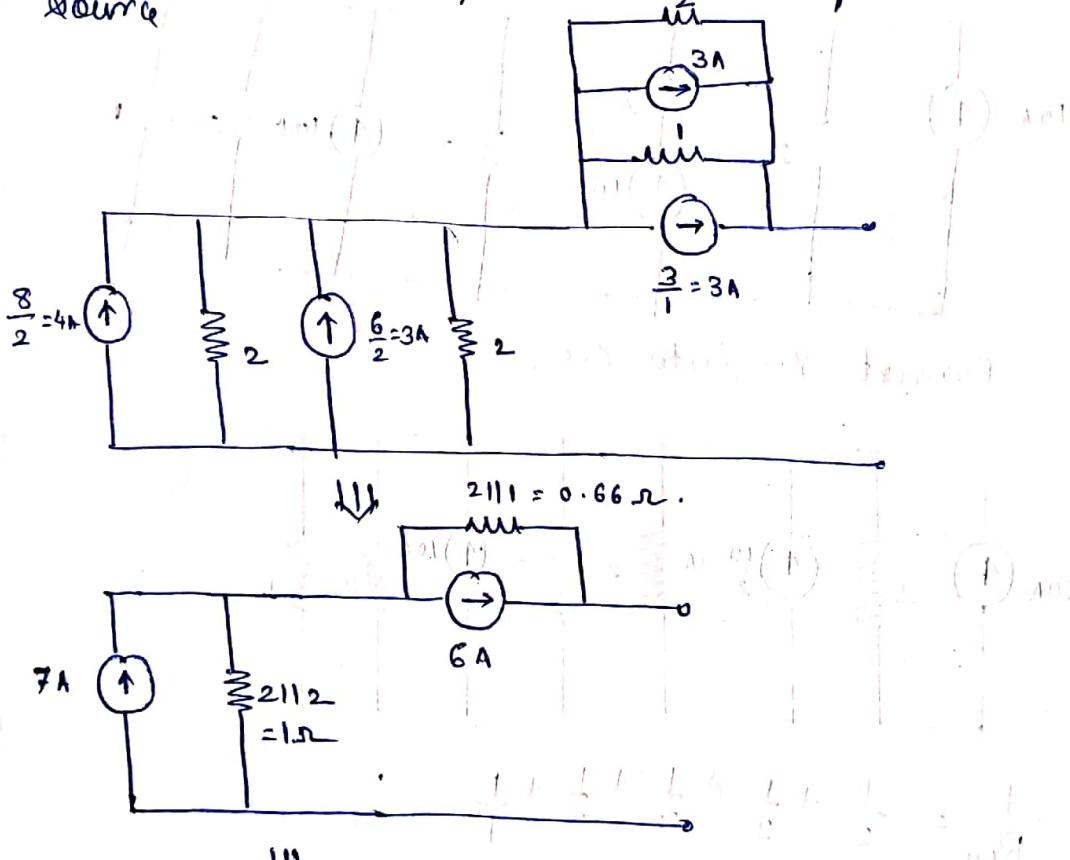Convert all Voltage source into Equivalent Current Source.







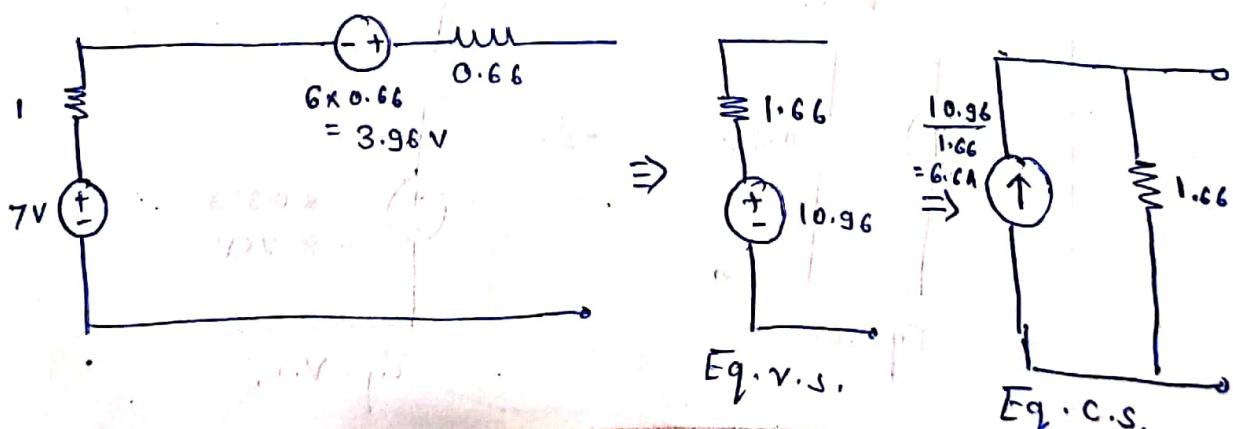↓
Convert current source into voltage source.





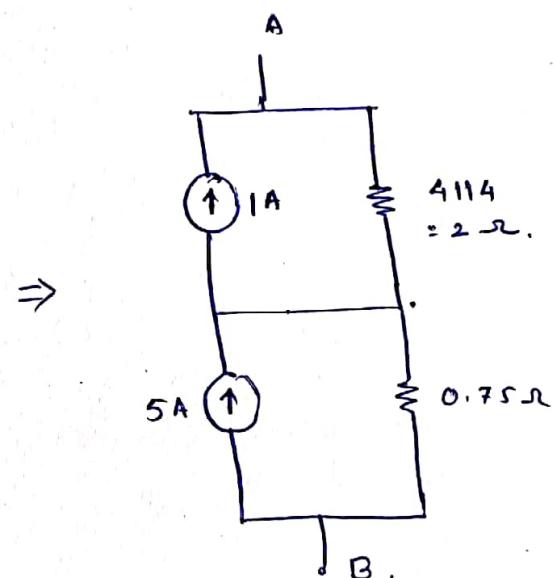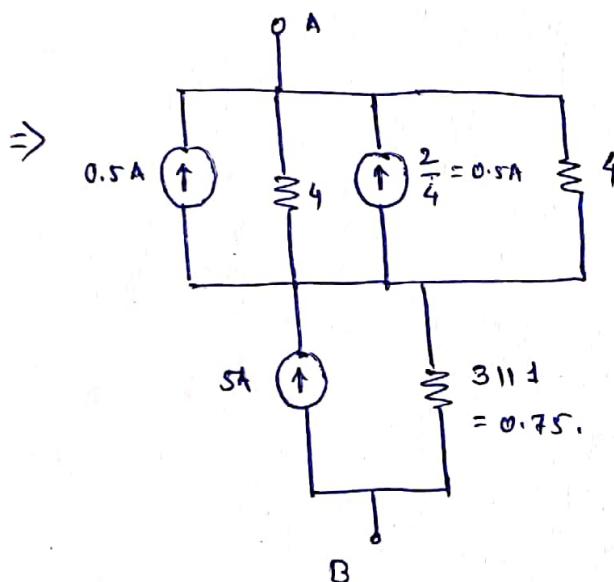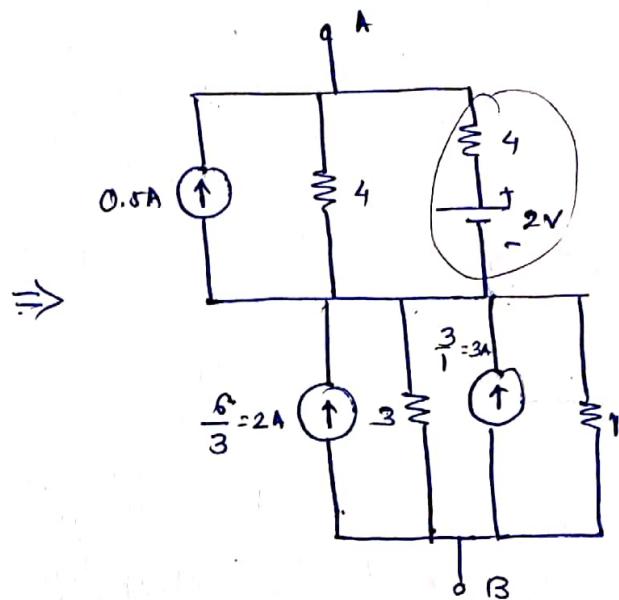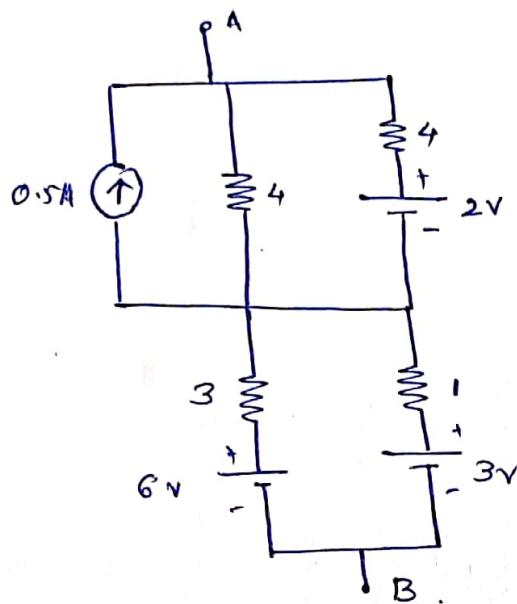7) Q.

Convert all voltage sources into single equivalent source.




Convert current source into voltage source, TS-2 ③

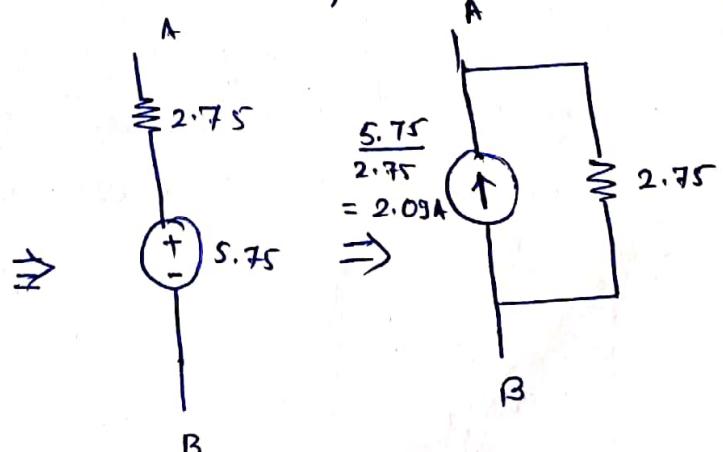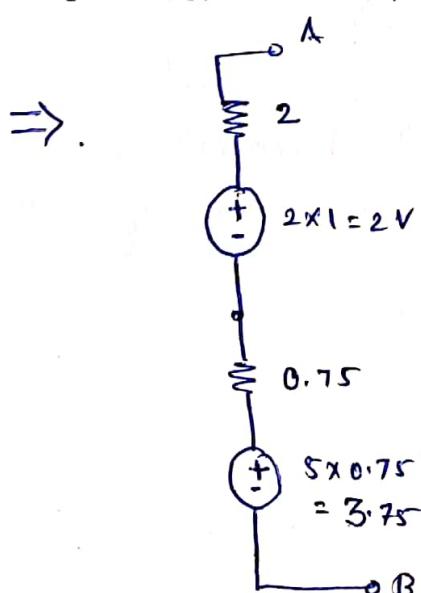

Eq. V.S.


W-15
Q.

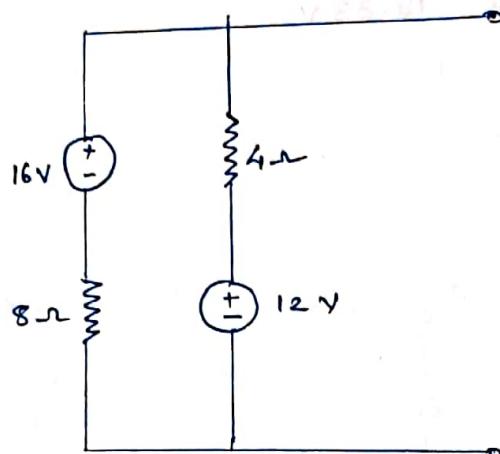using source Transformation, convert the circuit given below to a single voltage source in series with a resistor.




TS. 3 (1)

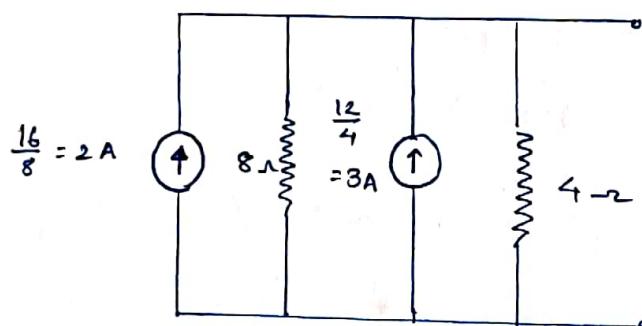=> Converting both Voltage source into its Equivalent Current Source.




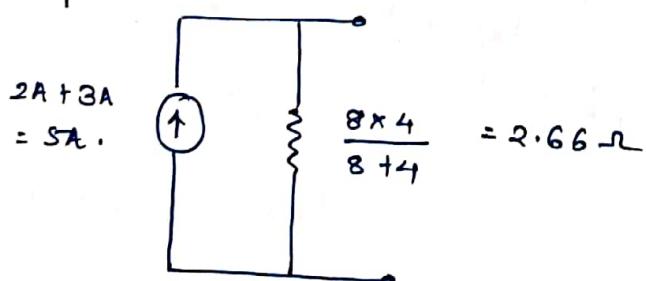Combining current source to convert into single Equivalent source.



Now, Convert current source into its Equivalent Voltage source in series with Resistance.

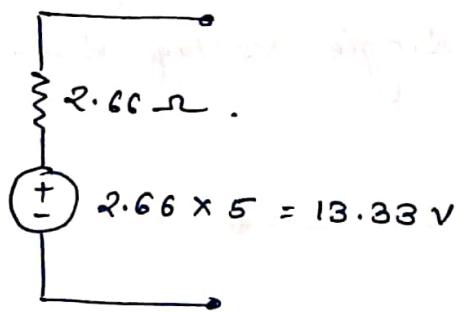∴ $\frac{V}{R} = \frac{13.33}{2.66 \Omega}$



∴ $\frac{V}{R} = \frac{13.33}{2.66 \Omega}$

∴ $I = \frac{13.33}{2.66 \Omega}$

∴ $I = 5 A$

∴ $V = I R$
∴ $V = 5 A \times 2.66 \Omega$

$$V = 5 A \times 2.66 \Omega$$
$$V = 13.33 V$$

∴ $V = 13.33 V$
∴ $V = 13.33 V$

$$V = 13.33 V$$
$$V = 13.33 V$$

∴ $V = 13.33 V$
∴ $V = 13.33 V$

49

Cramer's rule for solving simultaneous Equations

Equations

Suppose that the 'n' number of simultaneous Eqns are as follows.

$$a_{11}x_1 + a_{12}x_2 + \dots + a_{1n}x_n = c_1 \quad (1)$$

$$a_{21}x_1 + a_{22}x_2 + \dots + a_{2n}x_n = c_2 \quad (2)$$

$$a_{n1}x_1 + a_{n2}x_2 + \dots + a_{nn}x_n = c_n \quad (n)$$

then By Cramer's rule,

The value of unknown variables are as follows. ($a_{11}, a_{12}, \dots, a_{nn}$ & c_1, \dots, c_n are constant)

$$x_1 = \frac{\Delta_1}{\Delta}; \quad x_2 = \frac{\Delta_L}{\Delta}; \quad x_n = \frac{\Delta_n}{\Delta}$$

where Δ is the value of determinant of matrix form

$$\Delta = \begin{vmatrix} a_{11} & a_{12} & \dots & a_{1n} \\ a_{21} & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \dots & a_{nn} \end{vmatrix}$$

$$\Delta_{11} = \begin{vmatrix} c_1 & a_{12} & \dots & a_{1n} \\ c_2 & a_{22} & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ c_n & a_{n2} & \dots & a_{nn} \end{vmatrix}$$

$$\Delta_{21} = \begin{vmatrix} a_{11} & c_1 & \dots & a_{1n} \\ a_{21} & c_2 & \dots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & c_n & \dots & a_{nn} \end{vmatrix}$$

Kirchoff's laws:

Kirchoff discovered two basic laws that are used to calculate current in any branch & voltage across any branch.

- ① Kirchoff's voltage law (KVL)
- ② Kirchoff's current law (KCL)

① Kirchoff's voltage law (KVL)

Statement:


The algebraic sum of product of current & resistance of various branches of closed mesh of the circuit & emf in that closed mesh is equal to zero.
or.

The algebraic sum of the voltage around a close loop in a circuit must be equal to zero.


$$\sum IR + \sum EMF = 0$$

Rules Regarding KVL

①

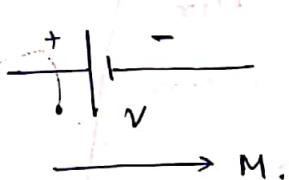


②

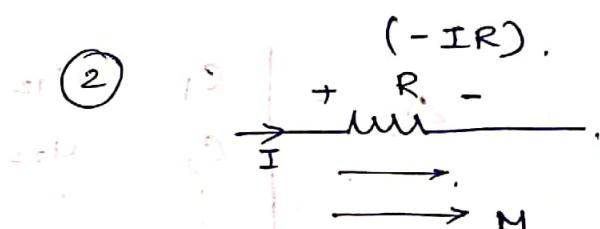


Fall in potential.

③

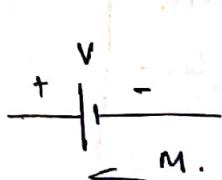


④

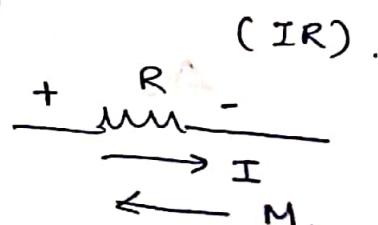


Rise in potential

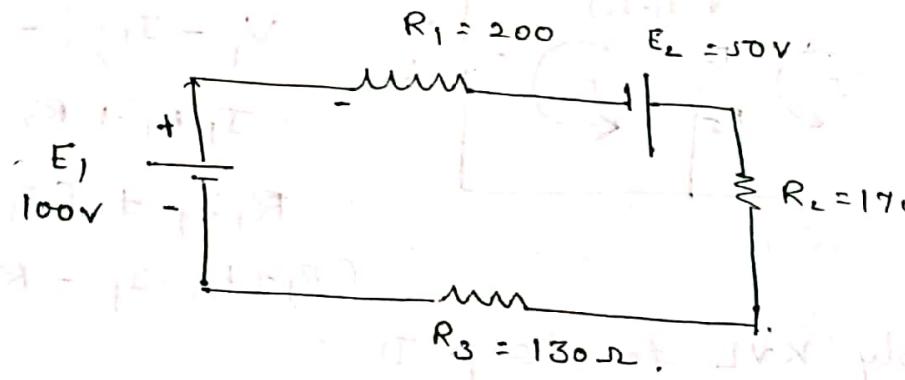Q. Integrate kvl loop equation with help of SI



\Rightarrow

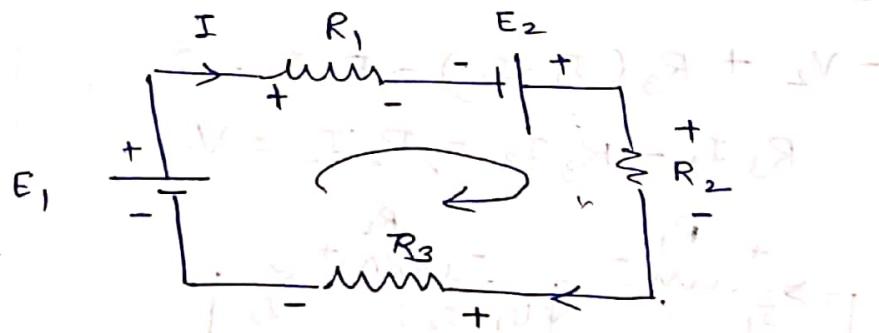

$$E_1 - IR_1 + E_2 - IR_2 - IR_3 = 0$$

$$\therefore E_1 + E_2 = IR_1 + IR_2 + IR_3$$


Rise in potential = fall in potential.

$$100 + 50 = I (200 + 170 + 130)$$

$$150 = I \times 500$$

$$I = \frac{150}{500} = 0.3 \text{Amp}$$

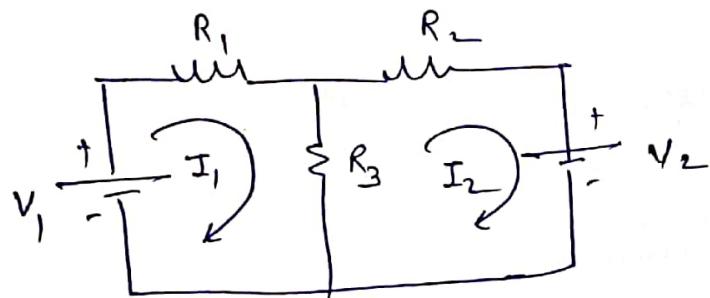Q. Apply KVL (mesh analysis) & write Equations.



$$V_1 - R_1 I_1 - R_3 (I_1 - I_2) = 0 \quad (1)$$

$$R_1 I_1 + (R_1 + R_3) I_1 - R_3 I_2 = V_1 \quad (1)$$

KVL to loop 2.

$$-R_3 (I_2 - I_1) - R_2 I_2 - V_2 = 0$$

$$R_3 I_2 - R_3 I_1 + R_2 I_2 + V_2 = 0 \quad (2)$$

$$-R_3 I_1 + (R_2 + R_3) I_2 = -V_2 \quad (2)$$

Matrix form.

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

By Cramer's Rule.

$$I_1 = \frac{\Delta_1}{\Delta} ; \quad I_2 = \frac{\Delta_2}{\Delta}$$

Where:

$$\Delta = \begin{vmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{vmatrix} ; \quad \Delta_1 = \begin{vmatrix} V_1 & -R_3 \\ -V_2 & R_2 + R_3 \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} R_1 + R_3 & V_1 \\ -R_3 & -V_2 \end{vmatrix}$$

For cross check:


$$\Delta = \begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix}$$

$R_{ii} \rightarrow$ sum of all Resistances in mesh i

$R_{ij} \rightarrow$ sum of Resistances common to mesh i & j

Q. Find Current in all Branches.

$$50 - 15 I_1 - 20(I_1 - I_2) = 0.$$

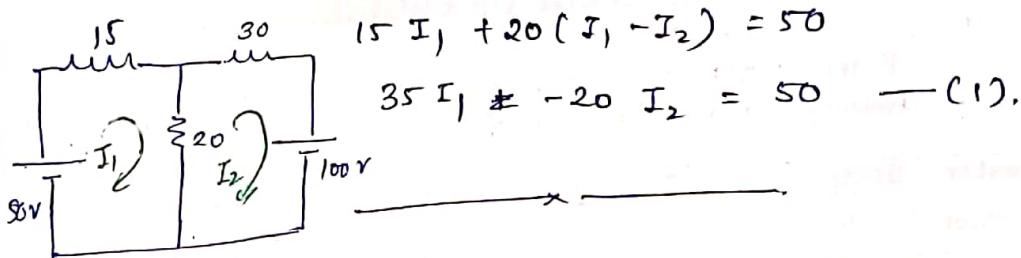

$$15 I_1 + 20(I_1 - I_2) = 50$$

$$35 I_1 + -20 I_2 = 50 \quad \text{--- (1)}$$

$$-20(I_2 - I_1) - 30 I_2 - 100 = 0.$$

$$20 I_2 - 20 I_1 + 30 I_2 = -100 \quad \text{--- (2)}$$

$$\Rightarrow -20 I_1 + 50 I_2 = -100 \quad \text{--- (3)}$$

$$\begin{bmatrix} 35 & -20 \\ -20 & 50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ -100 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = \begin{bmatrix} 35 & -20 \\ -20 & 50 \end{bmatrix} = 1350.$$

$$\Delta_1 = \begin{bmatrix} 50 & -20 \\ -100 & 50 \end{bmatrix} = 500.$$

$$I_1 = \frac{500}{1350} = 0.37 \text{ Amp.}$$


$$\Delta_2 = \begin{vmatrix} 35 & 50 \\ -20 & -100 \end{vmatrix} = -2500. \Rightarrow I_2 = \frac{-2500}{1350}. \\ I_2 = -1.85 \text{ Amp.}$$

Current through Middle Branch.

$$= I_1 - I_2 \Rightarrow 0.37 - (-1.85),$$

$$\Rightarrow 2.22 \text{ Amp.}$$

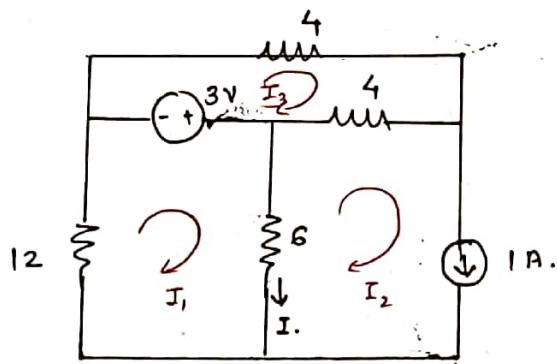Q In the given circuit, use Mesh analysis to obtain current I.



⇒ apply KVL in mesh ①

$$-12I_1 + 3 - 6(I_1 - I_2) = 0.$$

$$-12I_1 + 3 - 6I_1 + 6I_2 = 0.$$

$$-18I_1 + 6I_2 = -3$$

$$18I_1 - 6I_2 = 3 \quad (1)$$

Apply KVL in mesh ③.

~~$-6(I_2 - I_1) - 6(I_2 - I_3)$~~

$$-4I_3 - 4(I_3 - I_2) - 3 = 0.$$

$$-4I_3 - 4I_3 + 4I_2 - 3 = 0.$$

$$4I_2 - 8I_3 = 3.$$

$$-4I_2 + 8I_3 = -3 \quad (2).$$

We know. $I_2 = 1 \text{ Amp.}$

$$\textcircled{1} \Rightarrow 18I_1 - 6 = 3. \Rightarrow I_1 = \frac{9}{18} = 0.5 \text{ Amp.}$$

$$\textcircled{2} \Rightarrow -4(1) + 8I_3 = -3.$$


$$8I_3 = 1.$$

$$I_3 = 0.125 \text{ Amp.}$$

Current through 6Ω. $\Rightarrow I = I_2 - I_1 = 1 - 0.5.$

$I = 0.5 \text{ Amp}$

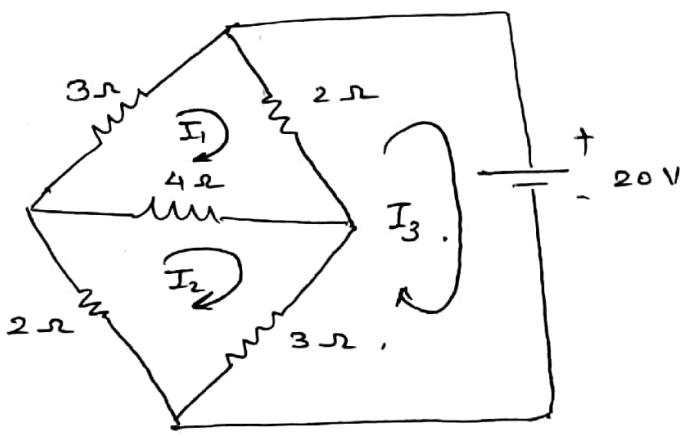Q. Using kirchoff's law, find the current through $4\ \Omega$ resistor



⇒ apply KVL in loop I.

$$-3I_1 - 2(I_1 - I_3) - 4(I_1 - I_2) = 0,$$

$$\underline{3I_1 + 2I_1 - 2I_3 + 4I_1 - 4I_2} = 0.$$

$$9I_1 - 4I_2 - 2I_3 = 0 \quad \text{--- (1)}$$

apply KVL in loop II.

$$-2I_2 - 4(I_2 - I_1) - 3(I_2 - I_3) = 0,$$

$$\underline{2I_2 + 4I_2 - 4I_1 + 3I_2 - 3I_3} = 0,$$

$$-4I_1 + 9I_2 - 3I_3 = 0 \quad \text{--- (2)}$$

apply KVL in loop III.

$$-20 - 3(I_3 - I_2) - 2(I_3 - I_1) = 0,$$

$$20 + 3I_3 - 3I_2 + 2I_3 - 2I_1 = 0,$$

$$-2I_1 - 3I_2 + 5I_3 = -20 \quad \text{--- (3)}.$$

In Matrix form,

$$\begin{bmatrix} 9 & -4 & -2 \\ -4 & 9 & -3 \\ -2 & -3 & 5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -20 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = \begin{vmatrix} 9 & -4 & -2 \\ -4 & 9 & -3 \\ -2 & -3 & 5 \end{vmatrix} = 160$$

$$\Delta_1 = \begin{vmatrix} 0 & -4 & -2 \\ 0 & 9 & -3 \\ -20 & -3 & 5 \end{vmatrix} = -600$$

$$\Delta_2 = \begin{vmatrix} 9 & 0 & -2 \\ -4 & 0 & -3 \\ -2 & -20 & 5 \end{vmatrix} = -700$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-600}{160} = -3.75; \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{-700}{160} = -4.375$$

$$\text{Current through } 4\Omega \Rightarrow I_2 - I_1$$

$$\Rightarrow -4.375 - (-3.75)$$

$$\Rightarrow -4.375 + 3.75$$

$$\Rightarrow -0.625 \text{ Amp.}$$

Or.

$$\text{Current through } 4\Omega \Rightarrow I_1 - I_2$$

$$\Rightarrow -3.75 - (-4.375)$$

$$\Rightarrow -3.75 + 4.375$$

$$\Rightarrow 0.625 \text{ Amp.}$$

Example 2.13

Analyse the circuit of Fig. 2.25 (a) by the mesh method. From the results, calculate the current in the 5Ω resistance.

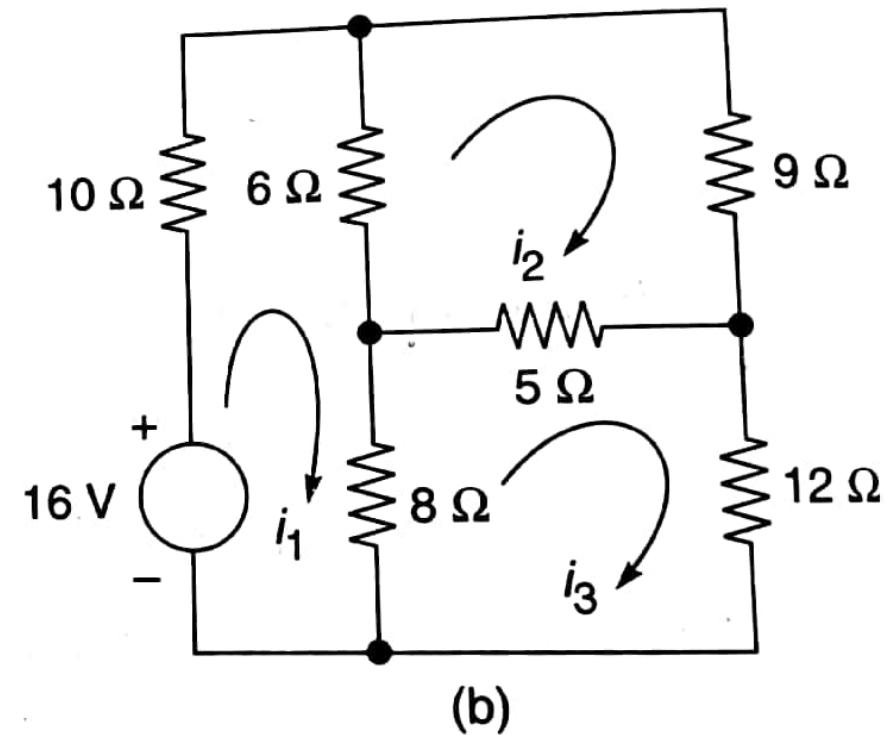
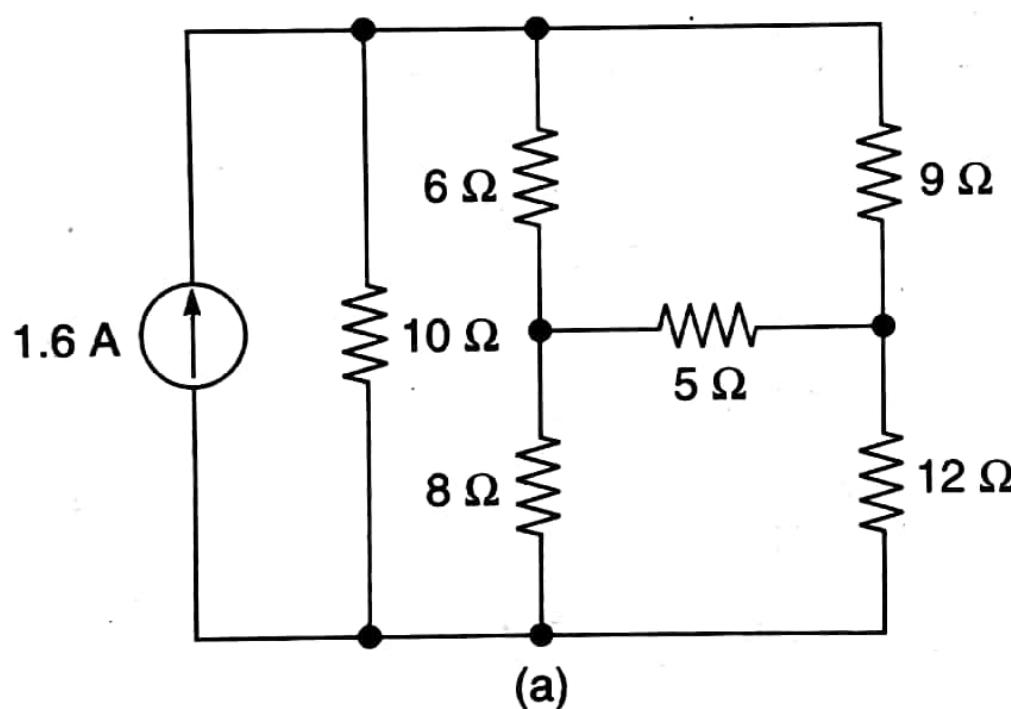


Fig. 2.25

Solution The practical current source of Fig. 2.25 (a) is first converted to voltage source as in Fig. 2.25 (b). Three meshes are immediately identified with associated currents i_1 , i_2 and i_3 . KVL equations for the three meshes are written as follows (directly in organized form).

$$\text{Mesh 1: } (10 + 6 + 8)i_1 - 6i_2 - 8i_3 = 16$$

$$\text{or, } 24i_1 - 6i_2 - 8i_3 = 16 \quad (\text{i})$$

$$\text{Mesh 2: } -6i_2 + (6 + 9 + 5)i_2 - 5i_3 = 0$$

$$\text{or, } -6i_1 + 20i_2 - 5i_3 = 0 \quad (\text{ii})$$

$$\text{Mesh 3: } -8i_3 - 5i_2 + (8 + 5 + 12)i_3 = 0$$

$$\text{or, } -8i_1 - 5i_2 + 25i_3 = 0 \quad (\text{iii})$$

Solving Eqs (i), (ii) and (iii)

$$i_1 = 0.869 \text{ A}, i_2 = 0.348 \text{ A} \text{ and } i_3 = 0.348 \text{ A}$$

$$\begin{aligned} \text{Current through } 5 \Omega \text{ resistance} &= i_2 - i_3 \\ &= 0 \text{ A} \end{aligned}$$

Resistances 6Ω , 8Ω , 9Ω and 12Ω form a *bridge*. When any resistance is connected across a *balanced bridge*, it will not carry any current. Also observe,

$$\frac{6\Omega}{8\Omega} = \frac{2}{3} = \frac{9\Omega}{12\Omega} = (\text{equal bridge arms ratio})$$

Example 2.14

For the circuit of Fig. 2.26 (a) determine the voltage v across 20Ω resistance using mesh analysis.

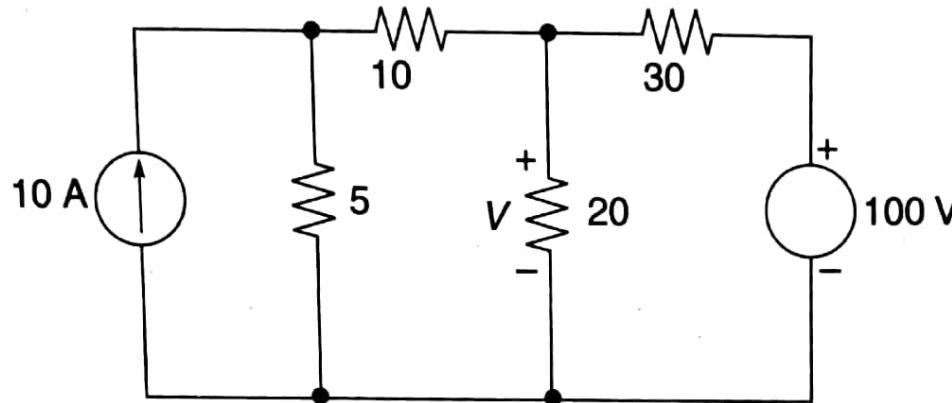


Fig. 2.26 (a)

Solution

Converting the practical current to a voltage source, we draw the circuit as in Fig. 2.26 (b). Writing the two mesh equations.

$$-50 + 15i_1 + 20(i_1 - i_2) = 0 \quad (i)$$

Or, $35i_1 - 20i_2 = 50 \quad (ii)$

$$20(i_2 - i_1) + 30i_2 + 100 = 0 \quad (iii)$$

Or, $-20i_1 + 50i_2 = -100 \quad (iv)$

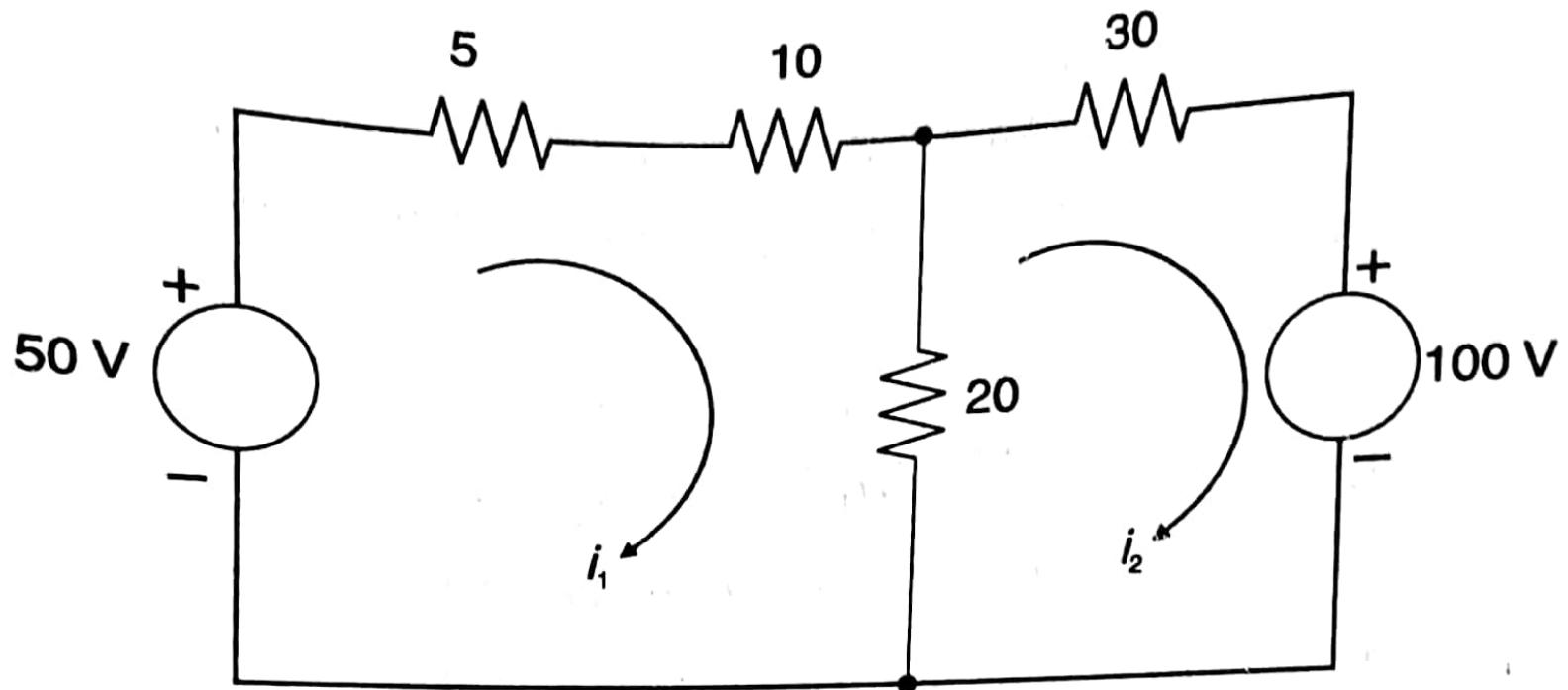


Fig. 2.26 (b)

Solving Eqs (ii) and (iv), we get

$$i_1 = 0.37 \text{ A}, \quad i_2 = -1.85 \text{ A}$$

Voltage across 20 Ω resistance

$$v = 20(i_1 - i_2) = 20 \times 2.22 = 44.4 \text{ V}$$

Example 2.10 Find the current through the 2Ω resistor.

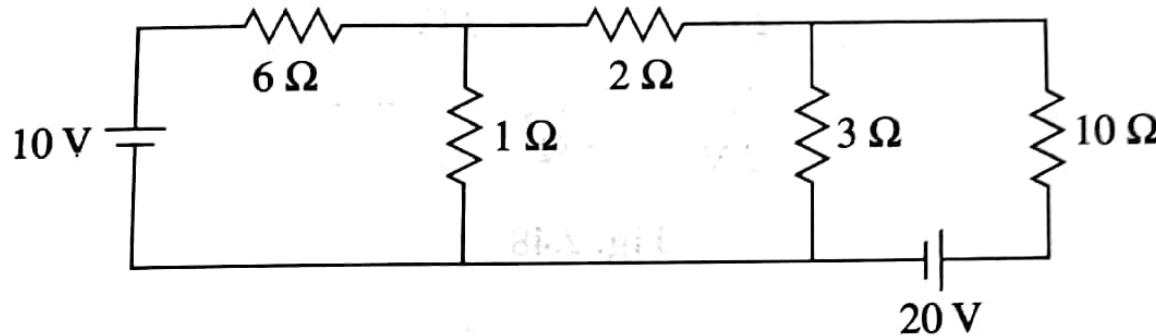


Fig. 2.46

Solution Assigning clockwise currents in three meshes,

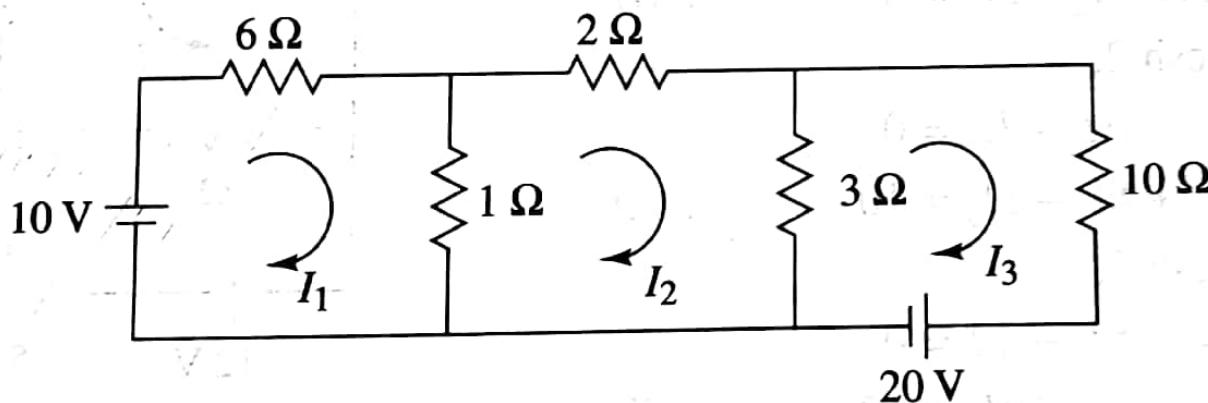


Fig. 2.47

Applying KVL to Mesh 1,

$$10 - 6I_1 - 1(I_1 - I_2) = 0 \\ 7I_1 - I_2 = 10$$

Applying KVL to Mesh 2,

$$-(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0 \\ -I_1 + 6I_2 - 3I_3 = 0$$

Applying KVL to Mesh 3,

$$-3(I_3 - I_2) - 10I_3 - 20 = 0 \\ -3I_2 + 13I_3 = -20$$

Writing equations in matrix form,

$$\begin{bmatrix} 7 & -1 & 0 \\ -1 & 6 & -3 \\ 0 & -3 & 13 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -20 \end{bmatrix}$$

Solving equations (i), (ii) and (iii),

$$I_1 = 1.34 \text{ A}$$

$$I_2 = -0.62 \text{ A}$$

$$I_3 = -1.68 \text{ A}$$

$$I_{2\Omega} = -0.62 \text{ A}$$

Example 2.11 Determine the current through the 5Ω resistor.

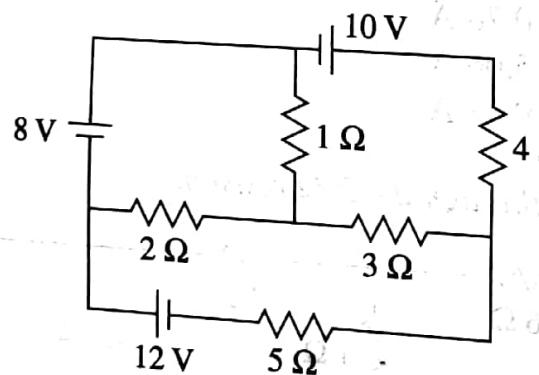


Fig. 2.48

Solution Assigning clockwise currents in three meshes,

Applying KVL to Mesh 1,

$$8 - 1(I_1 - I_2) - 2(I_1 - I_3) = 0$$

Applying KVL to Mesh 2,

$$3I_1 - I_2 - 2I_3 = 8 \quad \dots(i)$$


Applying KVL to Mesh 3,

$$-I_1 + 8I_2 - 3I_3 = 10 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$-2(I_3 - I_1) - 3(I_3 - I_2) - 5I_3 + 12 = 0 \quad \dots(iii)$$

$$-2I_1 - 3I_2 + 10I_3 = 12$$

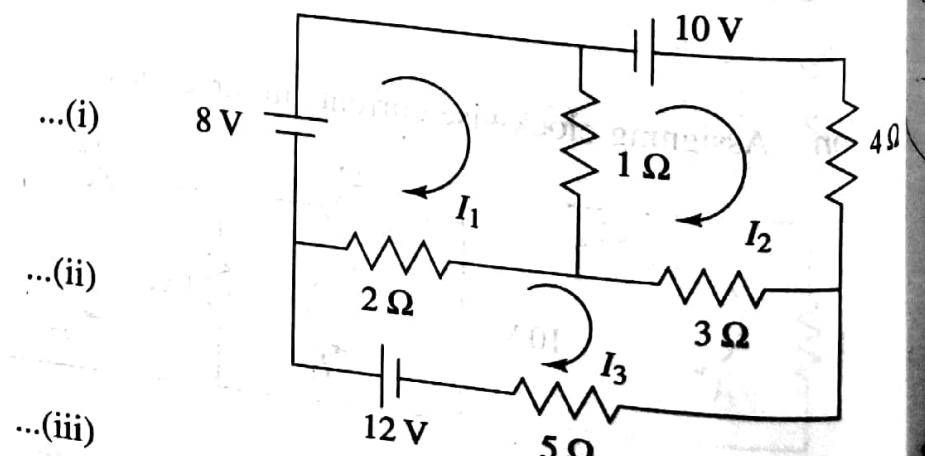

Writing equations in matrix form,

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 8 & -3 \\ -2 & -3 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 10 \\ 12 \end{bmatrix}$$

Solving equations (i), (ii) and (iii),

$$\begin{aligned} I_1 &= 6.01 \text{ A} \\ I_2 &= 3.27 \text{ A} \\ I_3 &= 3.38 \text{ A} \\ I_{5\Omega} &= 3.38 \text{ A} \end{aligned}$$

Example 2.12 Find the current supplied by the battery.

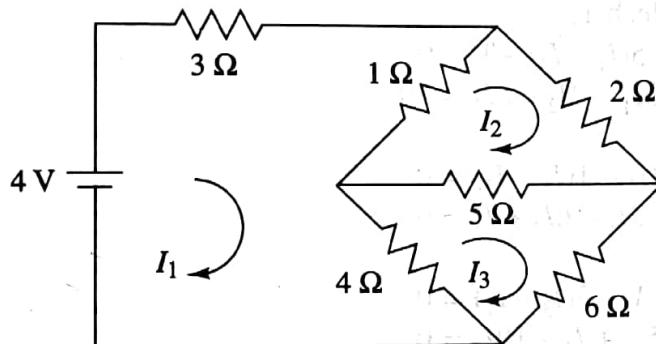


Fig. 2.50

Solution Applying KVL to Mesh 1,

$$4 - 3I_1 - 1(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$8I_1 - I_2 - 4I_3 = 4 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-2I_2 - 5(I_2 - I_3) - 1(I_2 - I_1) = 0$$

$$-I_1 + 8I_2 - 5I_3 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$-6I_3 - 4(I_3 - I_1) - 5(I_3 - I_2) = 0$$

$$-4I_1 - 5I_2 + 15I_3 = 0 \quad \dots(iii)$$

Writing equations in matrix form,

$$\begin{bmatrix} 8 & -1 & -4 \\ -1 & 8 & -5 \\ -4 & -5 & 15 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \\ 0 \end{bmatrix}$$

Solving equations (i), (ii) and (iii),

$$\begin{aligned} I_1 &= 0.66 \text{ A} \\ I_2 &= 0.24 \text{ A} \\ I_3 &= 0.26 \text{ A} \end{aligned}$$

Current supplied by the battery = 0.66 A.

Example 2.14 Find the current through the 2Ω resistor.

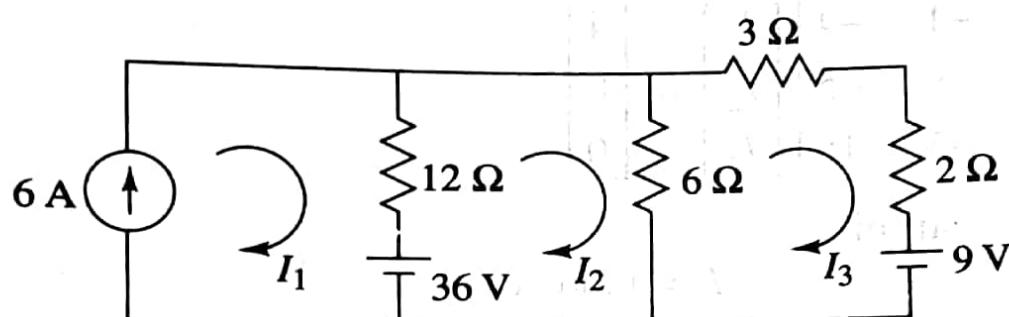


Fig. 2.52

Solution Mesh 1 contains a current source of 6 A. Hence, we cannot write KVL equation for Mesh 1. Since direction of current source and mesh current I_1 are same,

$$I_1 = 6 \text{ A}$$

Applying KVL to Mesh 2,

$$36 - 12(I_2 - I_1) - 6(I_2 - I_3) = 0$$

$$36 - 12(I_2 - 6) - 6I_2 + 6I_3 = 0$$

$$18I_2 - 6I_3 = 108$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_2) - 3I_3 - 2I_3 - 9 = 0$$

$$6I_2 - 11I_3 = 9$$

Solving equations (ii) and (iii),

$$I_3 = 3 \text{ A}$$

$$I_{2\Omega} = 3 \text{ A}$$

Kirchoff's current law:

Statement :


Sum of currents flowing into any node in the circuit is equal to sum of current coming out of the same node.

In other words, summation of all currents entering or leaving a node must be equal to zero.

$$\therefore \sum I = 0$$

Incoming current is considered as +ve.

Outgoing current is considered as -ve.

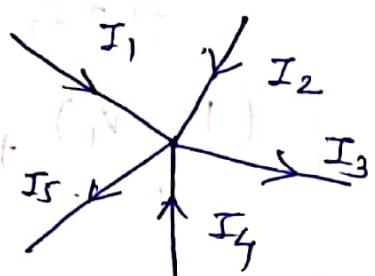


$$I_1 + I_2 + (-I_3) + (I_4) + (-I_5) = 0.$$

or

$$I_1 + I_2 + I_4 = I_3 + I_5.$$

Rules Regarding KCL

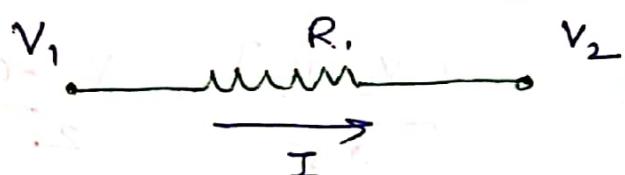


At Node 1

$$I = -\frac{(v_1 - v_2)}{R}$$


At Node 2,

$$I = \frac{v_1 - v_2}{R}$$

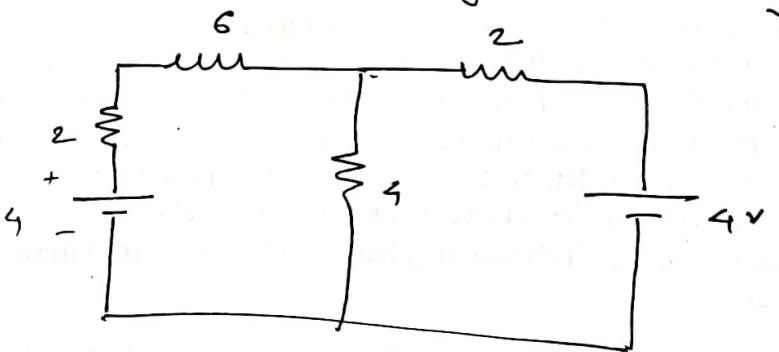Q. Find current through 6 Ω resistor. By nodal analysis



⇒

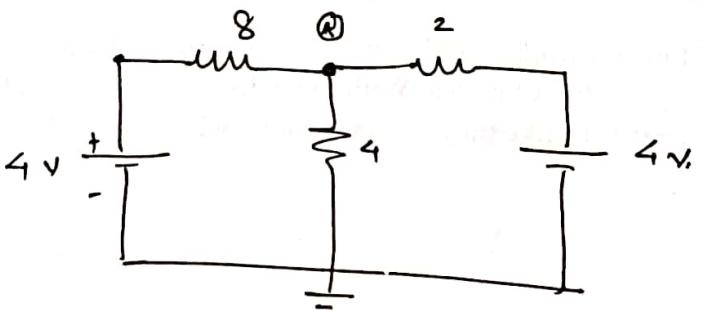

KCL at Node 8

$$\frac{V_A - 4}{8} + \frac{V_A}{4} + \frac{V_A - 4}{2} = 0$$

$$\frac{V_A - 4}{8} + \frac{2V_A}{8} + \frac{4V_A - 16}{8} = 0$$

$$V_A - 4 + 2V_A + 4V_A - 16 = 0$$

$$7V_A - 20 = 0$$


$$7V_A = 20 \Rightarrow V_A = 20/7 \text{ V.}$$

Current Through 6 Ω Resistor (I_1) = $\frac{V_A - 4}{8}$

$$= \frac{\frac{20}{7} - 4}{8} = \frac{\frac{20 - 28}{7}}{8}$$

$$= -\frac{8}{7} \times \frac{1}{8} = -\frac{1}{7} \text{ Amp.}$$

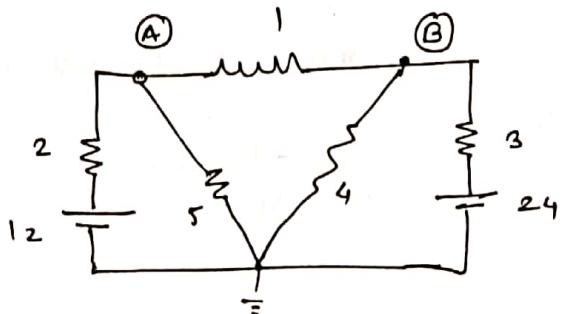Q. Write the Node Voltage Equation and determine current through 1Ω resistor



\Rightarrow Write KCL Equation for Node A

$$\frac{V_A - 12}{2} + \frac{V_A}{5} + \frac{V_A - V_B}{1} = 0$$

$$17V_A - 10V_B = 60 \quad (1)$$

Write KCL Eqn for Node B.

$$\frac{V_B - V_A}{1} + \frac{V_B}{4} + \frac{V_B - 24}{3} = 0$$

$$12V_A - 19V_B = -96 \quad (2)$$

$$\begin{bmatrix} 17 & -10 \\ 12 & -19 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 60 \\ -96 \end{bmatrix}$$


$$V_A = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} 60 & -10 \\ -96 & -19 \end{bmatrix}}{\begin{bmatrix} 17 & -10 \\ 12 & -19 \end{bmatrix}} = \frac{-1140 - 960}{-323 + 120} = \frac{-2100}{-203} = \frac{2100}{203}$$

$$V_A = \frac{2100}{203} = 10.34 \text{ V}$$

$$V_B = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 17 & 60 \\ 12 & -96 \end{bmatrix}}{\begin{bmatrix} 17 & -10 \\ 12 & -19 \end{bmatrix}} = \frac{-1632 - 720}{-203} = \frac{-2352}{-203} = 11.58 \text{ V}$$

$$\begin{aligned} \text{Current through } 1\Omega \text{ resistor} &= \frac{V_B - V_A}{1} = 11.58 - 10.34 \\ &= 1.24 \text{ Amp (from node B to A)} \end{aligned}$$

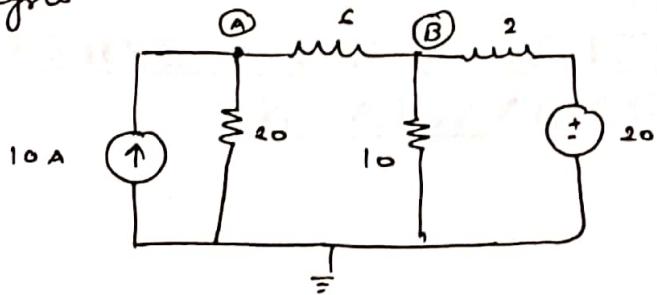Q Determine current in each branch of Resistor using nodal analysis (10 Ω resistor)



→ Writing KCL at Node A.

$$-10 + \frac{V_A - 0}{20} + \frac{V_A - V_B}{6} = 0.$$

$$13V_A - 10V_B = 600 \quad \text{--- (1)}$$

Write KCL at Node B

$$\frac{V_B - V_A}{6} + \frac{V_B}{10} + \frac{V_B - 20}{2} = 0. \quad \begin{cases} V_A = 67.47 \\ V_B = 27.71 \end{cases}$$

$$5V_A - 23V_B = -300 \quad \text{--- (2)}$$

$$\text{Current through } 20\Omega \text{ resistor} \Rightarrow I_1 = \frac{V_A - 0}{20} = 3.373$$

$$\text{6Ω resistor} \Rightarrow I_2 = \frac{V_A - V_B}{6} = \frac{67.47 - 27.71}{6}$$

$$I_2 = 6.627$$


$$\text{Current through } 10\Omega \text{ resistor} \Rightarrow I_3 = \frac{V_B}{10} = 2.77 \text{ A.}$$

$$\text{Current through } 2\Omega \text{ resistor} \Rightarrow I_4 = \frac{V_B - 20}{2} = \frac{27.71 - 20}{2}$$

$$I_4 = 3.855 \text{ Amp.}$$

M-19

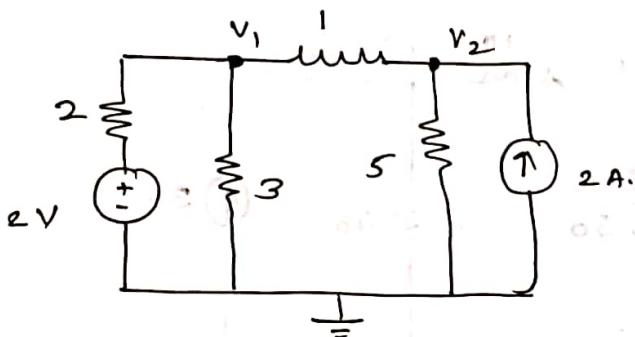Q. Write only Nodal equation of given circuit



⇒ apply KCL at node ①.

$$\frac{V_1 - 2}{2} + \frac{V_1}{3} + \frac{V_1 - V_2}{1} = 0$$

apply KCL at node ②.

$$\frac{V_2 - V_1}{1} + \frac{V_2}{5} - 2 = 0$$


$$① \Rightarrow 3V_1 - 6 + 2V_1 + 6V_1 - 6V_2 = 0$$

$$11V_1 - 6V_2 = 6 \quad (1)$$

$$② \Rightarrow 5V_2 - 5V_1 + V_2 - 10 = 0$$

$$-5V_1 + 6V_2 = 10 \quad (2)$$

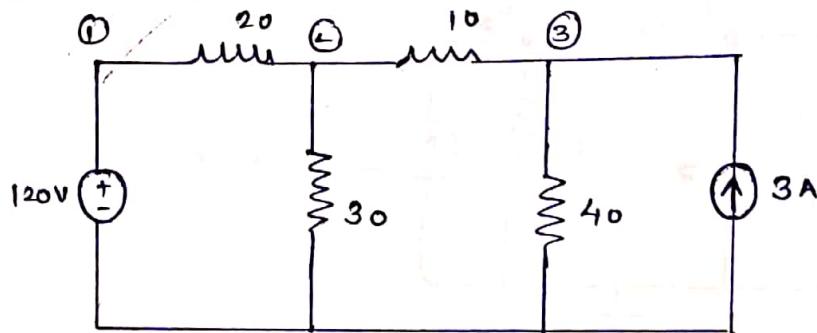Q Obtain Nodal voltages of node 1, 2 & 3 in the given circuit.



⇒ from the given figure;

$$V_1 = 120 \text{ V}.$$

Now, At Node ② ; apply KCL.

$$\frac{V_2 - 120}{20} + \frac{V_2}{30} + \frac{V_2 - V_3}{10} = 0.$$

$$3V_2 - 360 + 2V_2 + 6V_2 - 6V_3 = 0.$$

$$11V_2 - 6V_3 = 360 \quad (1).$$

At Node ③ ; apply KCL.

$$\frac{V_3 - V_2}{10} + \frac{V_3}{40} - 3 = 0.$$


$$4V_3 - 4V_2 + V_3 - 120 = 0.$$

$$-4V_2 + 5V_3 = 120 \quad (2)$$

$$\text{Now;} \quad V_2 = 81.29 \text{ V}.$$

$$V_3 = 89.03 \text{ V}.$$

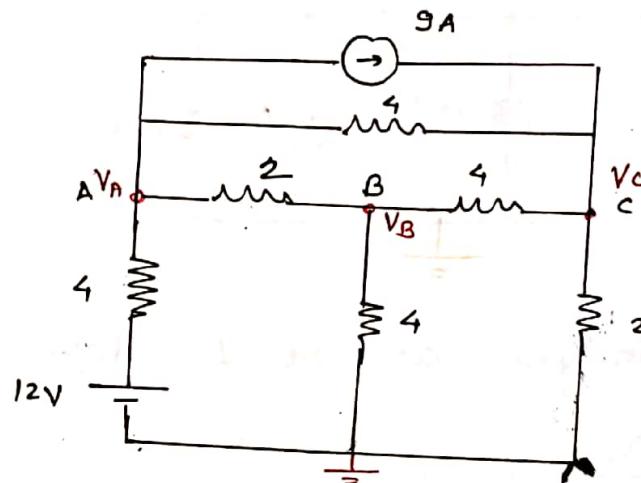- Q. Use nodal analysis to determine the voltage across BC and the current in the 12 V source.



At Node A; KCL eqn becomes.

$$\frac{V_A - 12}{4} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{4} + 9 = 0$$

$$V_A - 12 + \frac{1}{2}V_A - 2V_B + V_A - V_C = -36$$

$$4V_A - 2V_B - V_C = -24 \quad (1)$$

At Node B; KCL eqn becomes.

$$\frac{V_B - V_A}{2} + \frac{V_B - V_C}{4} + \frac{V_B}{4} = 0$$

$$2V_B - 2V_A + V_B - V_C + V_B = 0 \quad V_A = -4V$$

$$-2V_A + 4V_B - V_C = 0 \quad (2) \quad V_B = 0V$$

$$V_C = 8V$$

At Node C; KCL eqn becomes.

$$\frac{V_C - V_B}{4} + \frac{V_C - V_A}{4} + \frac{V_C}{2} - 9 = 0$$

$$V_C - V_B + V_C - V_A + 2V_C = 36$$

$$-V_A - V_B + 4V_C = 36 \quad (3)$$

$$V_{BC} = V_B - V_C$$

$$= 0 - 8$$

$$\boxed{V_{BC} = -8V}$$

Current


$$I = \frac{12 - V_A}{4} = \frac{12 - (-4)}{4}$$

$$I = \frac{16}{4} = 4 \text{ Amp.}$$

D-16.

Q

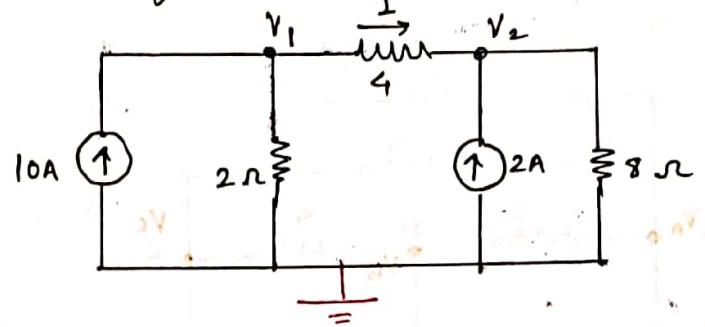User Nodal analysis, determine node voltages V_1, V_2 & current I for the circuit shown in figure.



⇒ By Nodal analysis, at Node 1 ; apply KCL.

$$-10 + \frac{V_1}{2} + \frac{V_1 - V_2}{4} = 0.$$

$$2V_1 + V_1 - V_2 = 20.$$

$$3V_1 - V_2 = 20 \quad (1)$$

at Node ② , apply KCL.

$$-\left(\frac{V_1 - V_2}{4}\right) + \frac{V_2}{8} - 2 = 0 \Rightarrow -2V_1 + 2V_2 + V_2 = 2 \times 8$$

$$-2V_1 + 3V_2 = 16$$

$$\cancel{2V_1 - 2V_2 + V_2 = 16}$$

$$\cancel{2V_1 - V_2 = 16} \quad (2) \quad 2V_1 - 3V_2 = -16 \quad (2)$$

$$V_1 = 4V. \quad 19.42V$$

$$V_2 = -8V. \quad 18.28V$$

current through 4Ω .,

$$I = \frac{V_1 - V_2}{4} = \frac{4 - (-8)}{4} = \frac{12}{4}$$

$$\boxed{I = 3 \text{ Amp}}$$

$$\boxed{I = 0.285 \text{ Amps}}$$

Superposition Theorem

The theorem is useful when a Network Contains more than one Energy Sources.

It is applicable to linear and bilateral N/w.

Linear N/w. A linear circuit is one whose Parameter is constant i.e. they do not change with voltage or current.

Bilateral N/w



A bilateral N/w is one whose properties or characteristics are same in either direction.

Statement

In a linear, bilateral Network, containing two or more sources, the response (current) in any Element is the algebraic sum of Current (response) caused by individual sources acting alone, while other sources are Inoperative and are replaced by their Internal resistances.


Note : In superposition theorem voltage source is short circuited because it has zero internal resistance ($R_i = 0$).

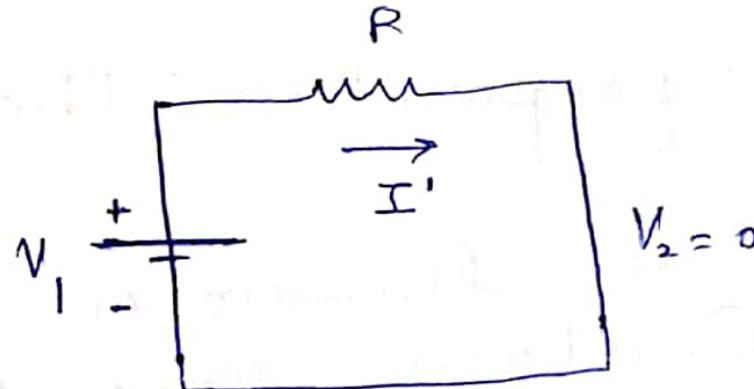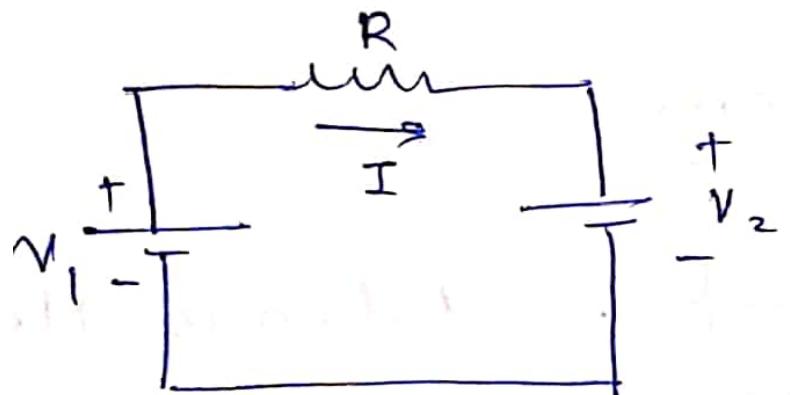• Current source is open circuited because it has infinite internal Resistance ($R_p = \infty$).



① when V_1 & V_2
both acting

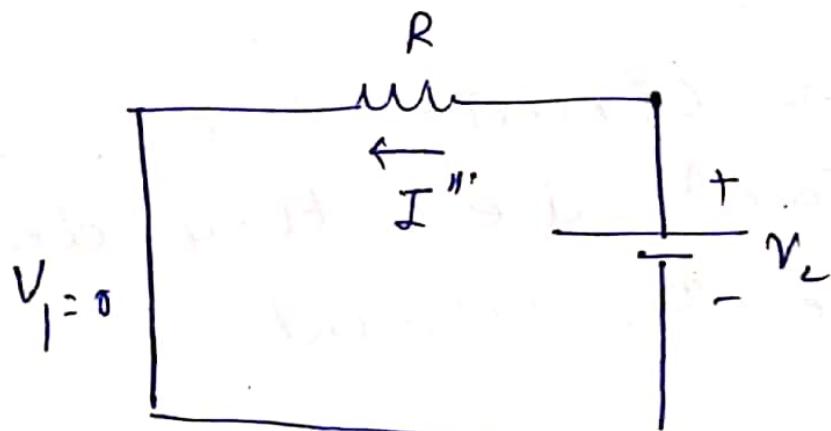② V_2 is replaced by zero
internal resistance
 V_1 is acting alone.



$$I = I' + I''$$

③ V_1 is short circuited
④ V_2 is acting alone.

Steps to Apply Superposition Theorem,

Step 1:

Select one Energy Source.

Step 2:

Replace all the other Energy source by their internal Resistance. (ie. Voltage Source is short circuited & current source is open circuited).

Step 3

With only one Energy source solve the circuit.

Step 4:


Repeat 1, 2, 3 steps for each source individually

(Take algebraic sum of current)

Step 5

Add algebraically the currents obtained due to the individual source to obtain the combine effect of all sources.

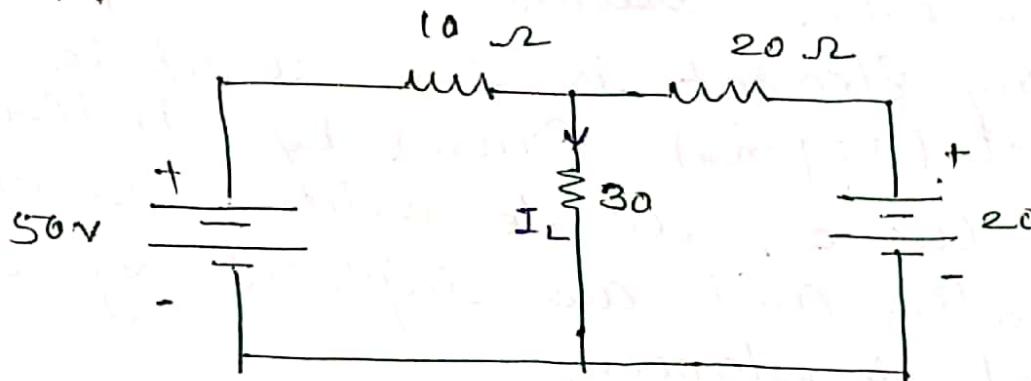Find I_L in circuit shown using superposition theorem.




By Superposition Theorem,

- a) Let's consider, 50V Source is active & Current through 30 Ω Resistor is I_L'

~~Total current~~

By current division Rule
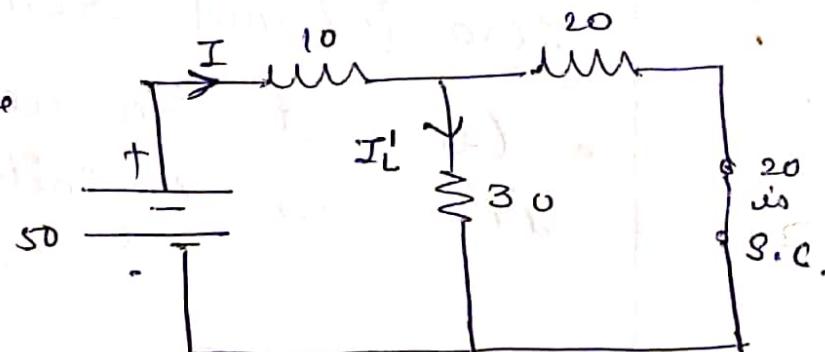
$$I_L' = \frac{20}{20+30} \times I_{\text{in}}$$



Now, Total current I ,

$$I = \frac{V}{R_T}$$

$$R_T = 10 + (20 || 30) = 10 + \frac{30 \times 20}{20+30} = 10 + \frac{600}{50}$$

$$\boxed{R_T = 22 \Omega}$$

Also,

$$I = \frac{50}{22} = 0.909 \text{ Amps } \downarrow$$

(b) Now, Let's consider, 20 V source is active & current through 30 Ω resistor is I_L''

∴ By current division Rule

$$I_L'' = \frac{10}{10+30} \times I.$$

Also,

$$I = \frac{V}{R_T}$$

$$R_T = 20 + (10 + 130) = 20 + \frac{10 \times 30}{10+30} = 20 + \frac{300}{40}$$

$$= 20 + 7.5 = 27.5$$


$$I = \frac{20}{27.5} = 0.73 \text{ Amps.}$$

$$I_L'' = \frac{10}{40} \times 0.73 = 0.181 \text{ A } \downarrow$$


Now, By Superposition theorem.

$$I_L = I_L' + I_L'' = 0.909 + 0.181$$

$$\boxed{I_L = 1.090 \text{ Amps}}$$

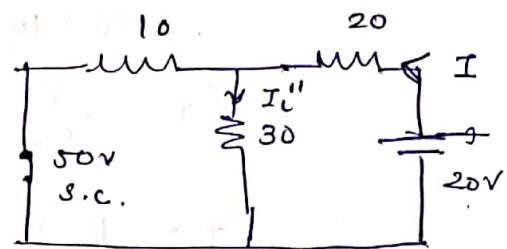

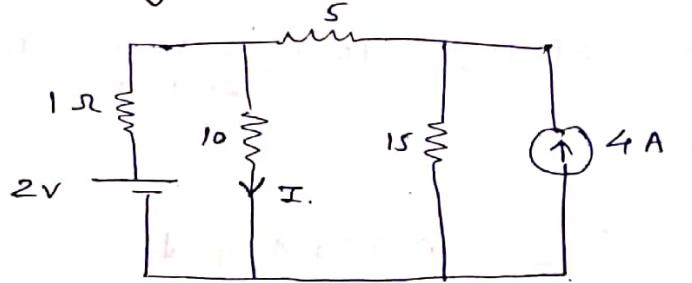Q. Solve for Power delivered to 10Ω by using SPT.



\Rightarrow when 2V is acting alone.


$$I' = \frac{20}{20+10} \times I_T$$

$$I_T = \frac{V}{R_T}$$

$$R_T = 1 + (10//20)$$

$$= 1 + \frac{10 \times 20}{30} = 1 + 6.67 = 7.67 \Omega$$
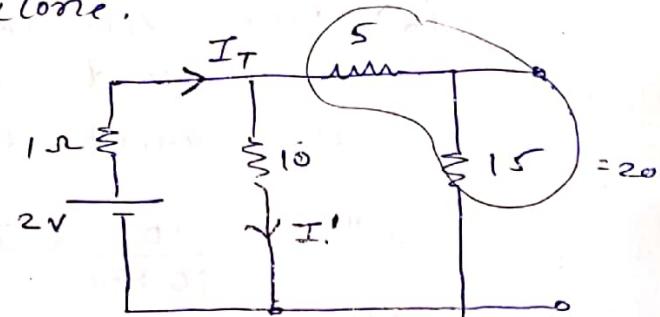
$$I_T = \frac{2}{7.67} = 0.17 \text{ Amp } (\downarrow)$$



when 4A is acting alone.


$$I'' = \frac{1}{10+1} \times I_A$$

$$I_A = \frac{15}{5.909 + 15} \times 4$$

$$I_A = 2.87 \text{ Amp}$$


$$I'' = \frac{1}{11} \times 2.87 = 0.26$$

$$I'' = 0.26 \text{ Amp } \downarrow$$

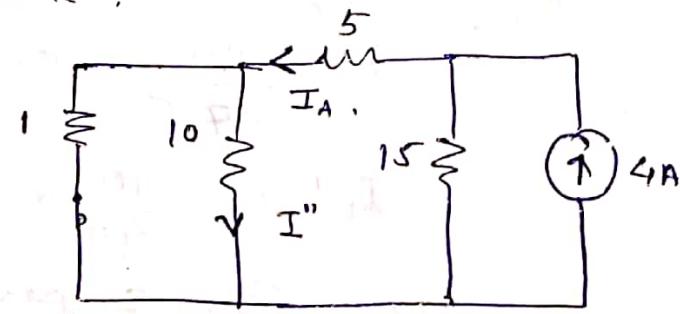

$$(10//1) \downarrow$$

$$= 0.909 \times 5 = 5.909$$

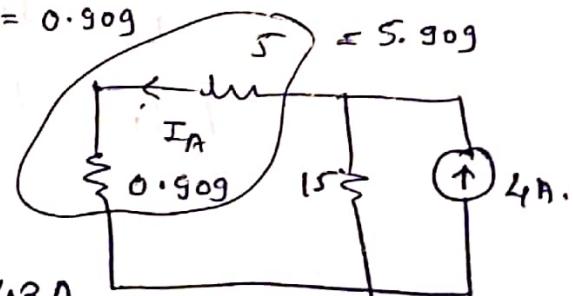


\therefore Current through 10Ω =

$$= 0.17 (\downarrow) + 0.26 (\downarrow) = 0.43 \text{ Amp}$$

$$\therefore \text{Power delivered to } 10\Omega = I^2 R = (0.43)^2 \times 10 \\ = 1.85 \text{ watts.}$$

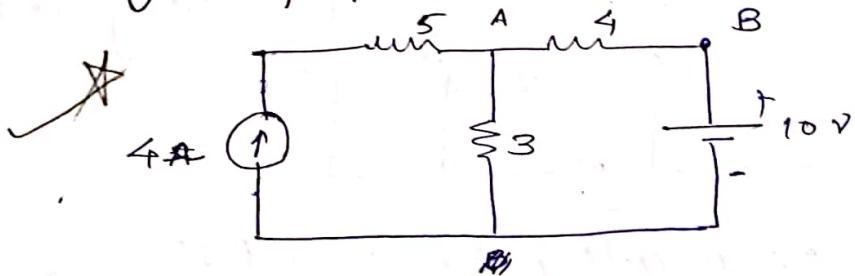Q. Find the voltage across Branch AB using superposition theorem. 83




\Rightarrow

When 4A is acting alone


$$I'_{AB} = \frac{3}{3+4} \times I$$
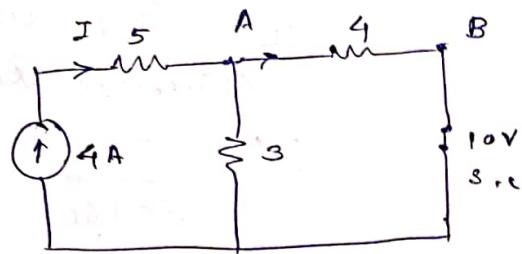
$$I'_{AB} = \frac{3}{7} \times 4 = 1.714 \text{ Amp.}$$



When 10V is acting alone.
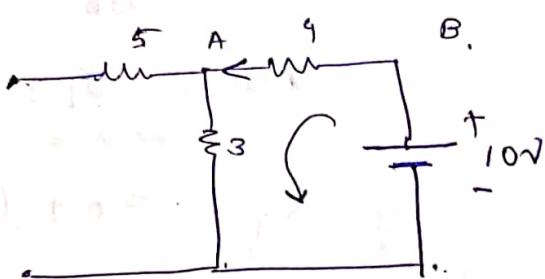
$$I''_{AB} = \frac{10}{4+3} = 1.429 \text{ Amp.}$$



Total Current I_{AB} by Superposition Theorem.


$$I_{AB} = I'_{AB} + I''_{AB} = 1.714 + (-1.429)$$

$$= 1.714 - 1.429 = 0.285 \text{ Amp.} (\rightarrow)$$

Direction of current is from A to B.

Q.

W-1X

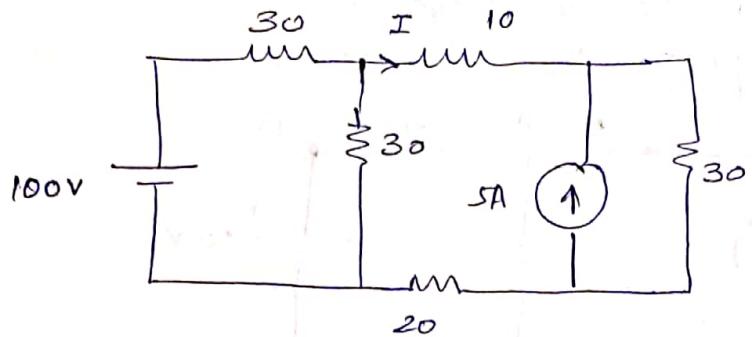

Find current 'I'
using SPT.

→ only 100V is acting find current I'

I_{L1} By current division Rule

$$I' = \frac{30}{30+60} \times I_L$$

$$I' = \frac{30}{60} \times I_L$$

Also, $I_L = \frac{V}{R_T}$

$$R_T = 30 + (30//60) = 30 + \frac{30 \times 60}{30+60} = 50 \Omega$$

$$I_L = \frac{100}{50} = 2 \text{ Amp.}$$

$$I' = \frac{2}{3} = 0.66 \text{ Amp } (\rightarrow)$$

only SA is acting alone find I''

$$I'' = \frac{30}{30+10+15+20} \times 5$$

$$I'' = \frac{30}{75} \times 5$$

$$I'' = 2 \text{ Amp } (\leftarrow)$$




∴ Total current.

$$I = I' + I''$$


$$= 0.66 + (-2)$$

$$\underline{I = -1.33 \text{ Amp.}}$$

$$I = 1.33 \text{ Amp } (\leftarrow)$$

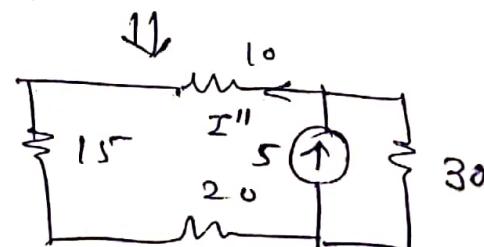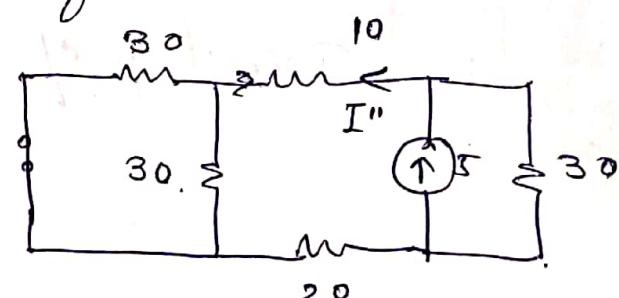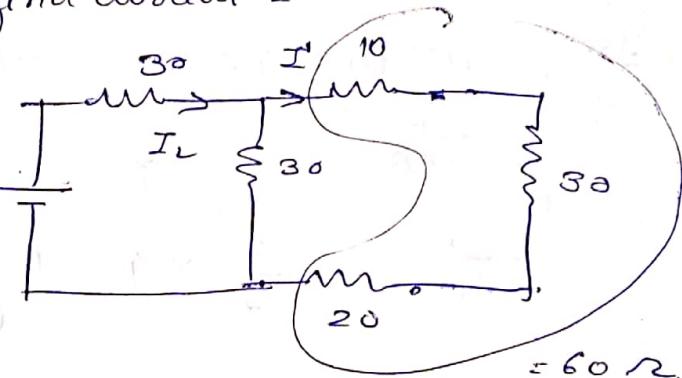

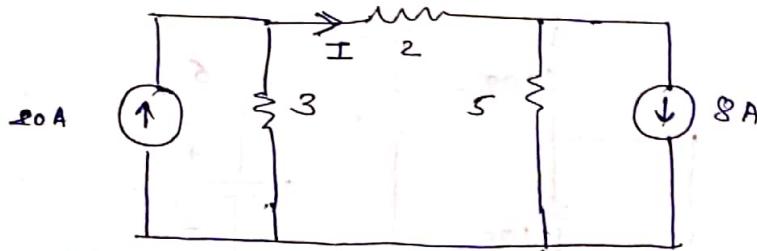Q. Calculate value of current through 2Ω resistor. using SPT.




\Rightarrow Consider, $20A$ is acting alone.
Find I'

$$I' = \frac{3}{3+2+5} \times 20$$

(By Current division Rule).
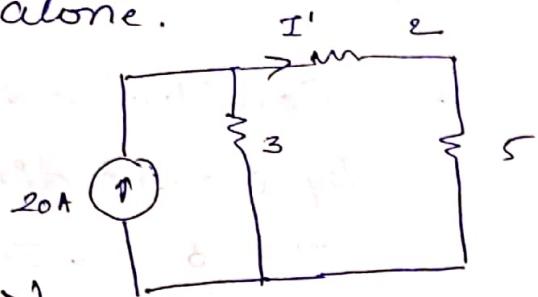
$$I' = \frac{3}{10} \times 20 = 6 \text{ Amp } (\rightarrow)$$




Consider $8A$ is acting alone.

Find I''

$$I'' = \frac{5}{3+2+5} \times 8$$
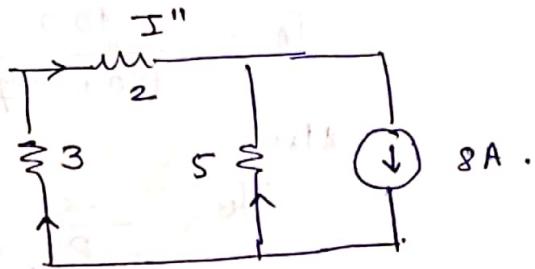
$$I'' = \frac{5}{10} \times 8 = 4 \text{ Amp } (\rightarrow)$$




Total current I through 2Ω is

$$I = I' + I'' = 6 + 4 = 10 \text{ Amp } (\rightarrow)$$

$$\boxed{I = 10 \text{ Amp } (\rightarrow)}$$

Q.
S-15,
S-17

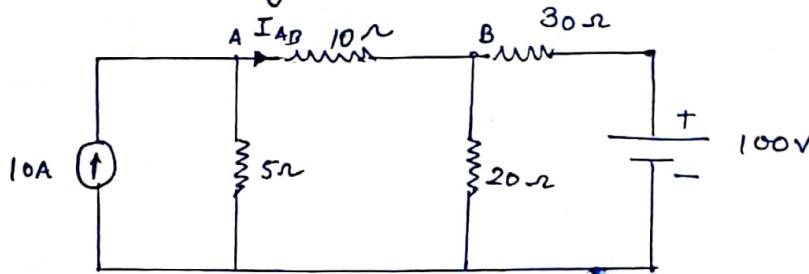
Find current through branch AB as shown in fig.



Sol:

- 1] When only 10A is acting alone
 30Ω & 20Ω are in parallel

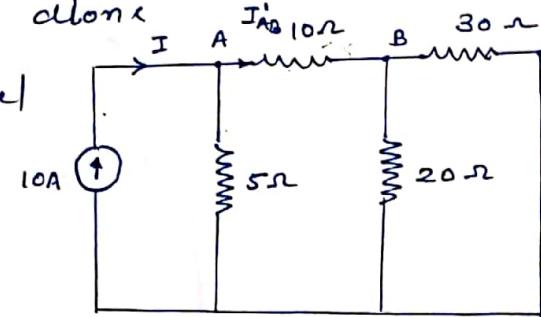
$$30 \parallel 20 = \frac{30 \times 20}{30 + 20} = 12\Omega$$



By current division Rule,

$$I_{AB}' = \frac{5 \times 10}{(5+10+12)}$$
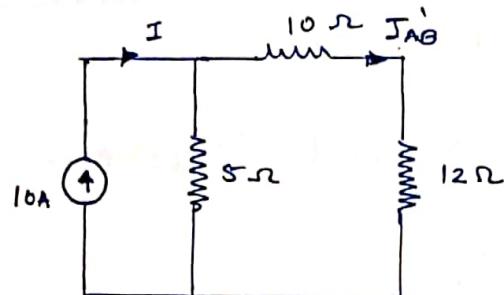
$$\underline{I_{AB}' = 1.85 A (\rightarrow)}$$




- 2] When 100V is acting alone

$$(10+5) \parallel 20$$

$$\therefore 15 \parallel 20 = \frac{15 \times 20}{15 + 20} = 8.57\Omega$$
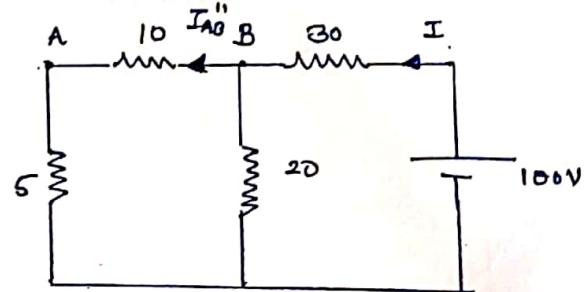
$$\therefore I = \frac{100}{30 + 8.57} = 2.59 A.$$



By current division Rule,


$$I_{AB}'' = \left(\frac{20}{20+15} \right) \times 2.59 = \underline{1.48 A (\leftarrow)}$$

$$\therefore \text{Current through } 10\Omega = I_{AB} = 1.85 (\rightarrow) - 1.48 (\leftarrow)$$


$$I_{AB} (\rightarrow) = 1.85 - 1.48$$

$$\boxed{I_{AB} (\rightarrow) = 0.37 A}$$

Q) Using superposition Theorem, find the current I in given figure.

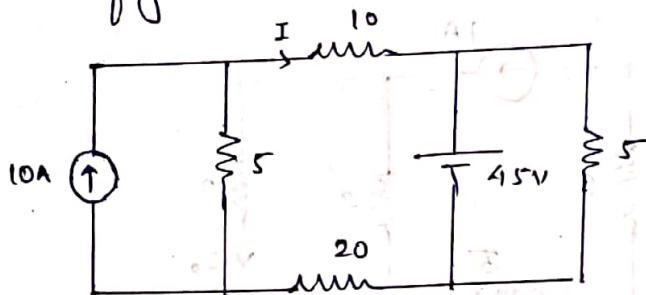


Case 1: When 10A is active alone.

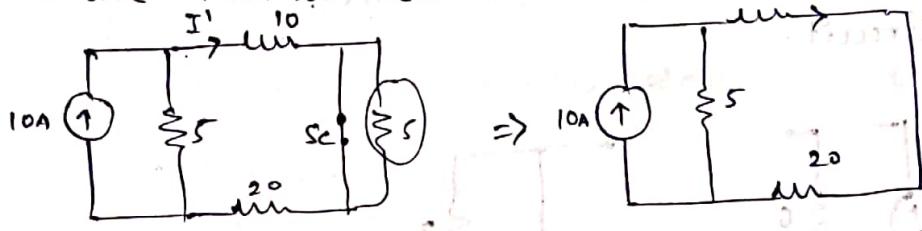

By current division Rule.

$$I' = \left(\frac{5}{5+30} \right) \times 10 = \frac{5}{35} \times 10 \Rightarrow I' = 1.42 \text{ Amp.} \quad (\rightarrow)$$

Case 2: When 45V is active alone.

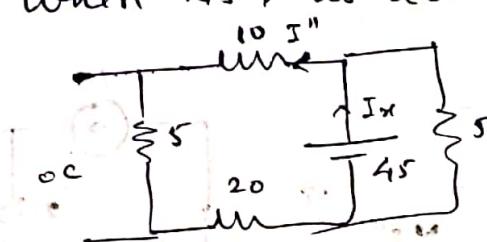

By current division Rule;

$$I'' = \left(\frac{5}{5+35} \right) \times I_x = (1).$$

Now; In above circuit


$$5 \parallel 35 = \frac{35 \times 5}{5+35} \Rightarrow R_{eq} = 4.375 \Omega.$$

$$45 \parallel 4.375 \Rightarrow I_x = \frac{45}{4.375} = 10.285 \text{ Amp.}$$

$$I'' = \frac{5}{40} \times 10.285 \Rightarrow I'' = 1.285 \text{ Amp.} \quad (\leftarrow)$$


$$\text{By SPT} \Rightarrow I = I' - I'' = 1.42 - 1.285 \\ I = 0.135 \text{ Amp.}$$

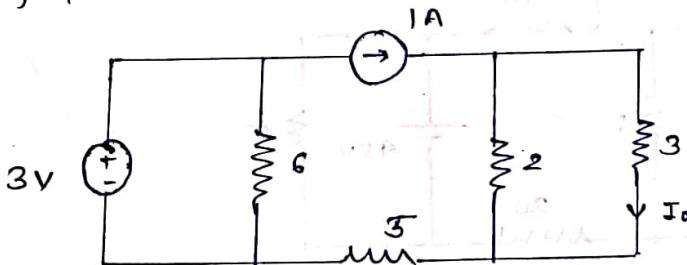- Q. Find current I_o (current through 3Ω) using Superposition Theorem.



→ Case 1: When 3V is active alone.


Redraw circuit:

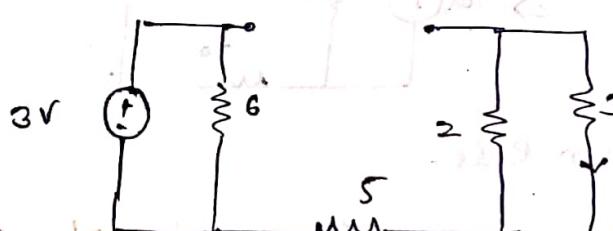

$$I_o' = 0 \text{ Amp.}$$

Case 2: When 1A is active alone.

Redraw circuit:

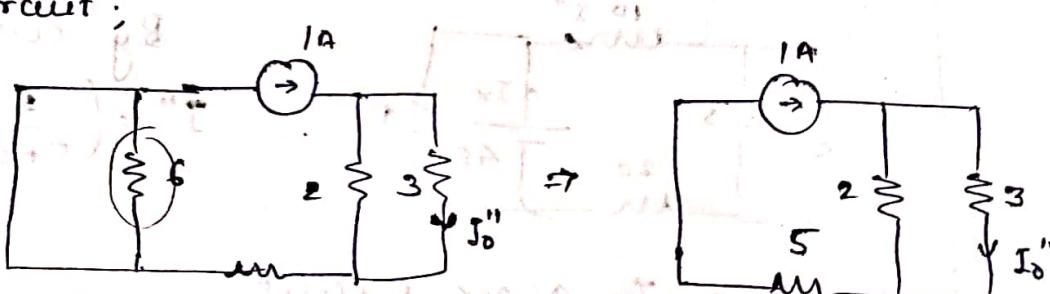

By current division Rule,


$$I_o'' = \left(\frac{2}{2+3} \right) \times 1 = \frac{2}{5} \times 1$$

$$I_o'' = 0.4 \text{ Amp (down)}.$$


By SPT

$$I_o = I_o' + I_o'' = 0.4 \text{ Amp (down)}.$$

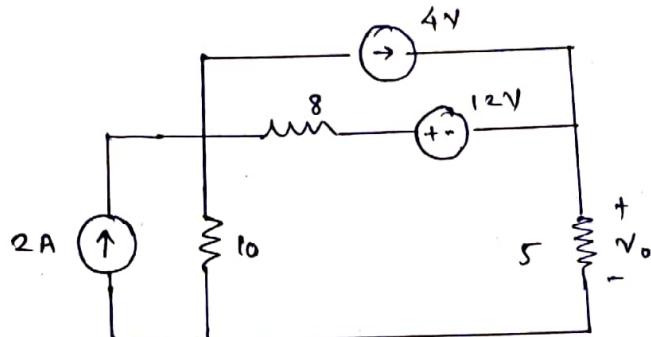Q. Use superposition to find V_o in the circuit given below.



→ Case 1: only 2 A is active alone.

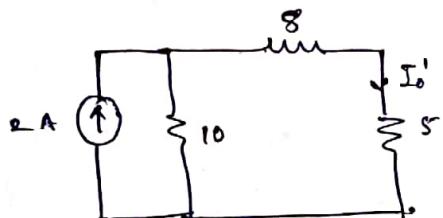


By current division Rule,

$$I_o' = \left(\frac{10}{10+15} \right) \times 2$$

$$I_o' = 1.538 \text{ A } (\downarrow)$$

Case 2: only 4 A is active alone

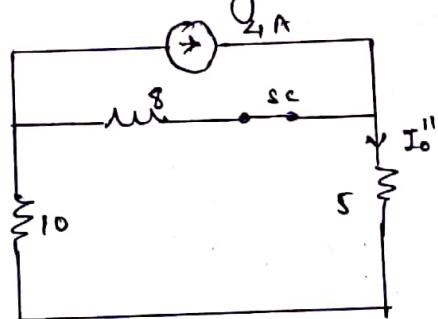


By current division Rule,

$$I_o'' = \left(\frac{8}{8+15} \right) \times 4$$

$$I_o'' = 2.133 \text{ A } (\downarrow)$$

Case 3: only 12V is active alone.

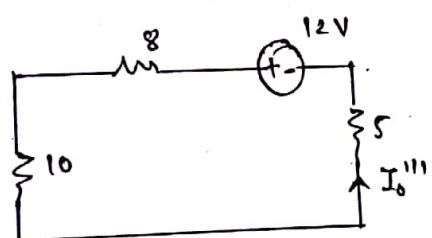

$$\text{Now: } I_o''' = \frac{12}{23}$$

$$I_o''' = 0.521 \text{ A } (\uparrow)$$


Now; By S.P.T.

$$I_o = I_o' + I_o'' - I_o''' = 1.538 + 2.133 - 0.521$$

$$I_o = 3.15 \text{ Amp } (\downarrow)$$





$$\text{Now: } V_o = I_o \times 5 \Rightarrow \boxed{V_o = 15.75 \text{ V}}$$

Therenin's Theorem.

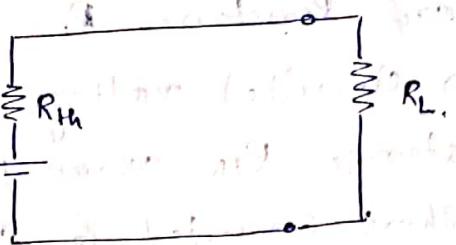

It states that current in any branch (may be R_L) in the network is same as would be obtained if R_L were supplied by voltage source V_{th} or V_{th} in series with Equivalent Resistance R_{th} ; V_{th} or V_{oc} being the open-circuited voltage at the terminals from which R_L is removed & R_{th} is the resistance of Network measured between two terminals with R_L removed & voltage source is replaced by its internal Resistance (S.C) & current source is replaced by Open Circuited.

Eg.

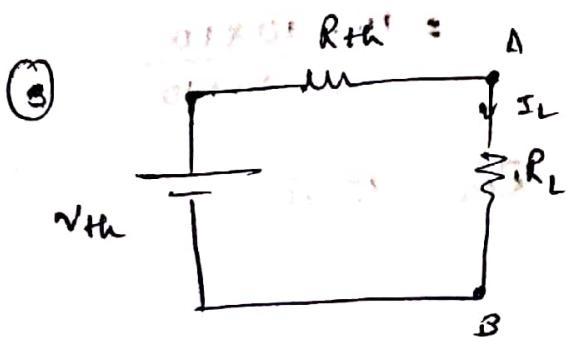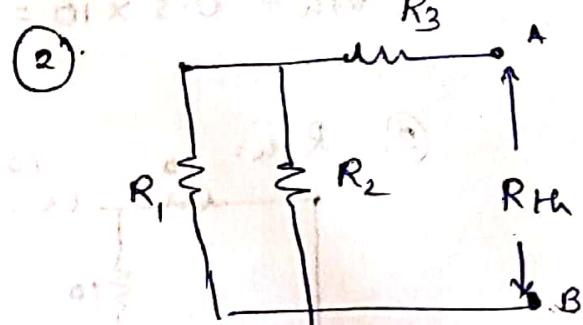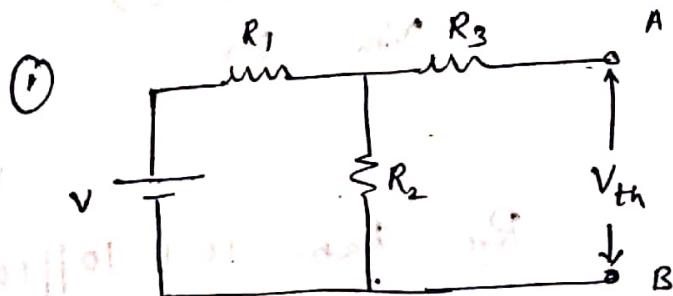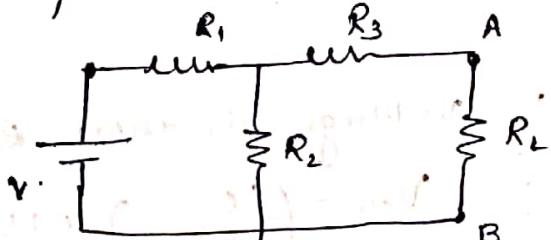

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


— (ohms law)

Steps to be followed in Thvenin's Theorem.

- ① Remove the load Resistance R_L
- ② find the open circuited voltage V_{th} across points A & B
- ③ find the Resistance R_{th} across points A & B.
also v_s is short circuited & C.S is open circuited
- ④ Replace Network by a voltage source V_{th} in series with Resistance R_{th}
- ⑤ Find the current through R_L using ohm's law

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

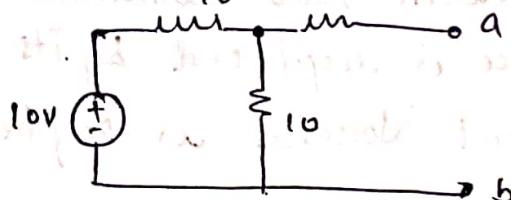- ⑥ Determine V_{th} & R_{th} across terminals AB.



$$\textcircled{1} \quad V_{th} = V_{ab}$$


$$I = \frac{10}{10+10} = 0.5 \text{ Amp.}$$

$$V_{th} = 0.5 \times 10 = 5 \text{ V.}$$

Voltage division Rule.

$$V_{th} = \left(\frac{10}{10+10} \right) \times 10$$

$$V_{th} = 5 \text{ V.}$$

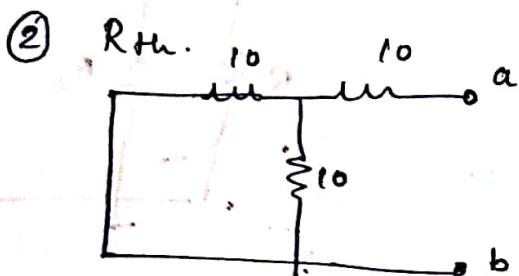


$$R_{th} = R_{ab} = 10 + 10 \parallel 10$$


$$= 10 + \frac{10 \times 10}{10+10}$$

$$R_{th} = 15 \Omega.$$

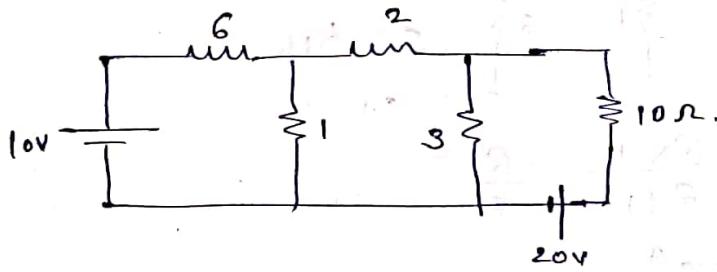Q. Find the current through 10Ω Resistor using Thvenin's Theorem.



Step 1: $V_{Th} = ?$

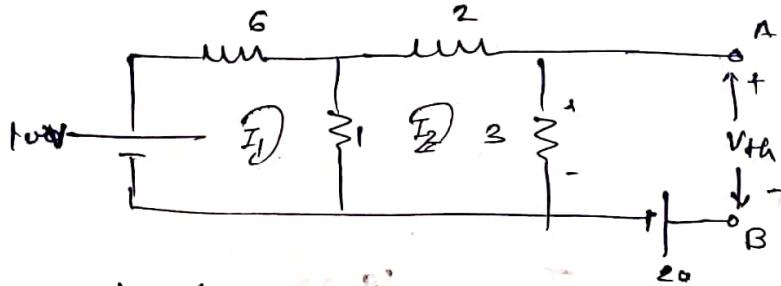

Apply KVL in Mesh 1.

$$10 - 6I_1 - 2(I_1 - I_2) = 0.$$

$$7I_1 - I_2 = 10 \quad \dots (1)$$

Apply KVL in Mesh 2.

$$-(I_2 - I_1) - 2I_2 - 3I_2 = 0.$$

$$I_1 - 6I_2 = 0. \quad \dots (2)$$

From (1) & (2); we get

$$I_1 = \quad \quad \quad I_2 = 0.24 \text{ A.}$$

Writing V_{Th} Eqn.


$$3I_2 - V_{Th} - 20 = 0.$$

$$V_{Th} = 3(0.24) - 20$$


$$V_{Th} = -19.28 \text{ V.}$$

$V_{Th} = 19.28 \text{ V}$ (B is at higher potential w.r.t A)

Step 2 : Calculation of R_{th}

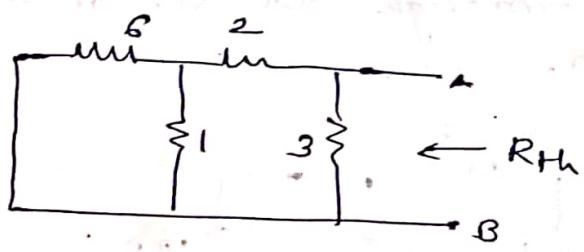

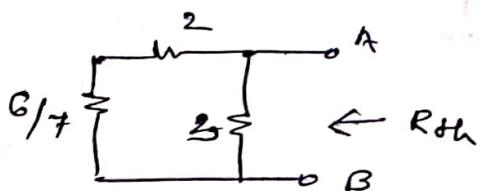
$$G \parallel 1 = \frac{G \times 1}{G + 1} = \frac{6}{6+1} = \frac{6}{7}$$




$$R_{th} = 1.47 \Omega$$

Step 3 : Calⁿ of I_L .

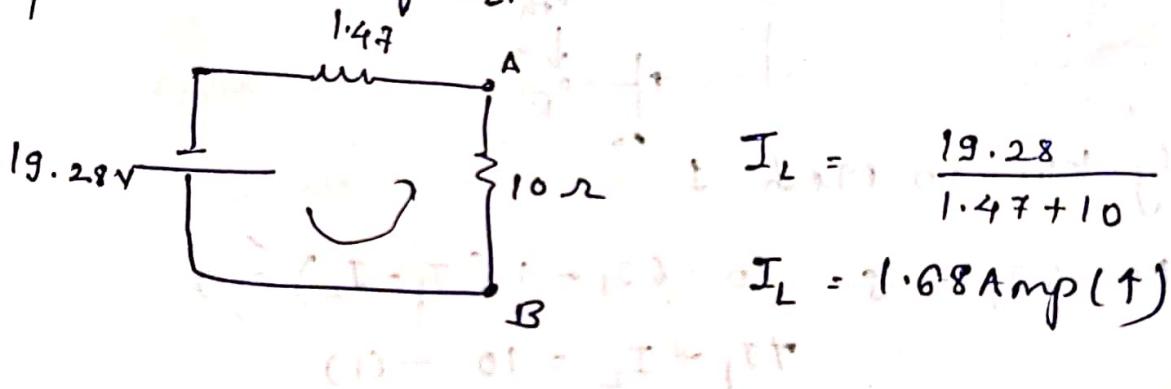

$$I_L = \frac{19.28}{1.47 + 10}$$
$$I_L = 1.68 \text{ Amp} (\uparrow)$$

Step 3: Calculation of I_L

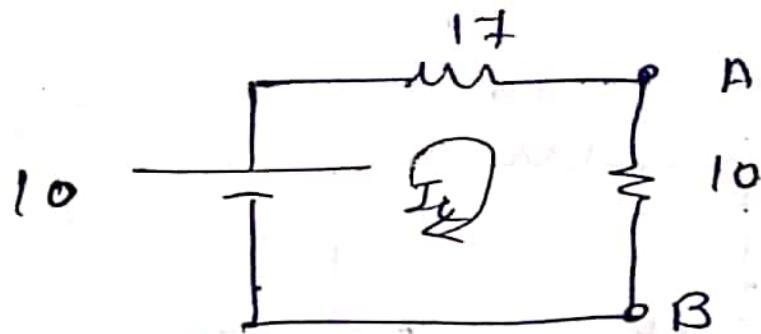

$$I_L = \frac{10}{17 + 10} = 0.37 \text{ Amps.}$$

Example 3.22

Find the current through the 10- Ω resistor.

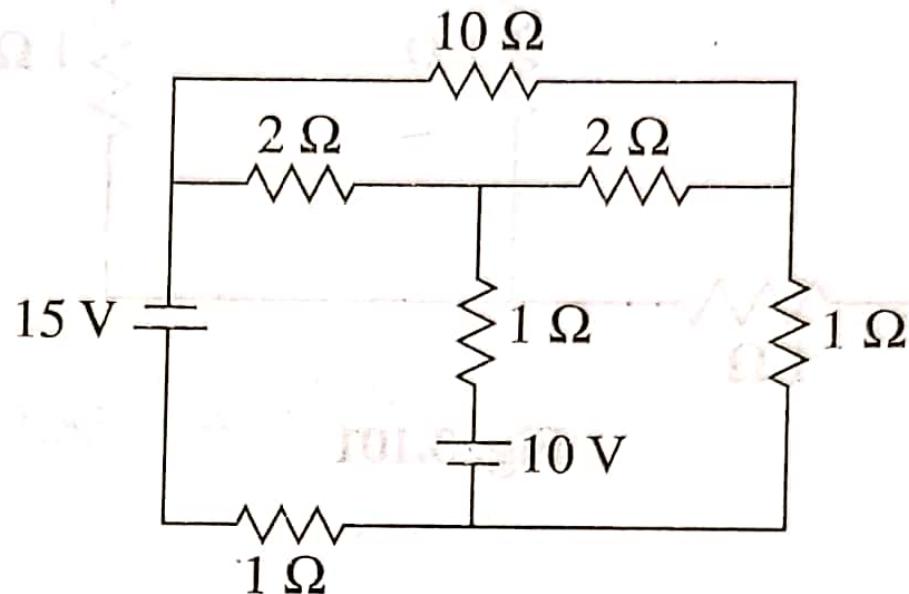


Fig. 3.99

Step I: Calculation of V_{Th}

Removing the 10Ω resistor from the network,

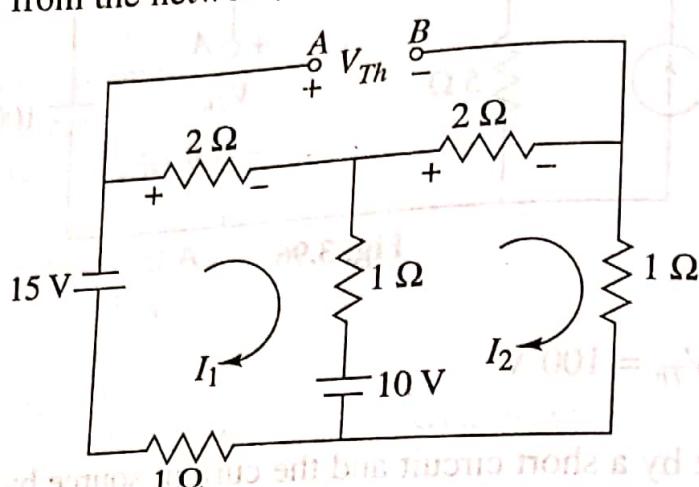


Fig. 3.100

Applying KVL to Mesh 1,

$$-15 - 2I_1 - 1(I_1 - I_2) - 10 - 1I_1 = 0 \\ 4I_1 - I_2 = -25$$

Applying KVL to Mesh 2,

$$10 - (I_2 - I_1) - 2I_2 - I_2 = 0 \\ -I_1 + 4I_2 = 10$$

Solving Eqs (1) and (2),

$$I_1 = -6 \text{ A}$$

$$I_2 = 1 \text{ A}$$

Writing V_{Th} equation,

$$-V_{Th} + 2I_2 + 2I_1 = 0$$

$$V_{Th} = 2I_1 + 2I_2 \\ = 2(-6) + 2(1) = -10 \text{ V}$$

= 10 V (the terminal B is positive w.r.t. A)

Step II: Calculation of R_{Th}

Replacing voltage sources by a short circuit,

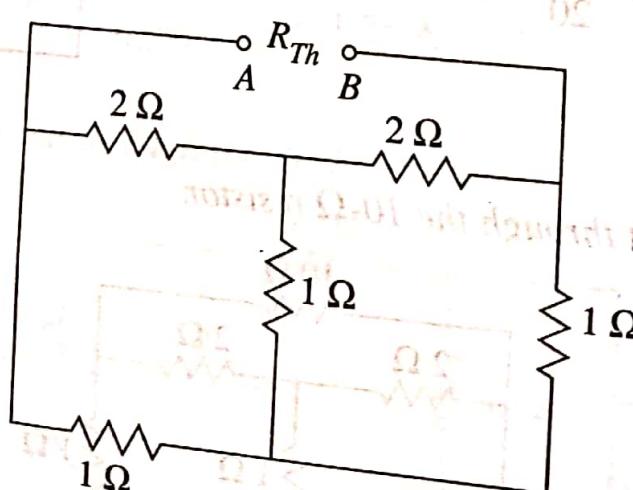


Fig. 3.101

Converting the star network formed by resistances of $2\ \Omega$, $2\ \Omega$ and $1\ \Omega$ into an equivalent delta network.

$$R_1 = 2 + 2 + \frac{2 \times 2}{1} = 8\ \Omega$$

$$R_2 = 2 + 1 + \frac{2 \times 1}{2} = 4\ \Omega$$

$$R_3 = 2 + 1 + \frac{2 \times 1}{2} = 4\ \Omega$$

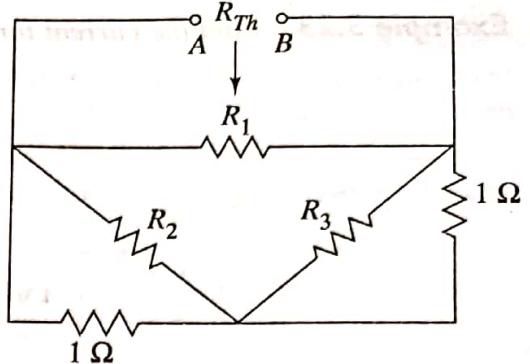


Fig. 3.102

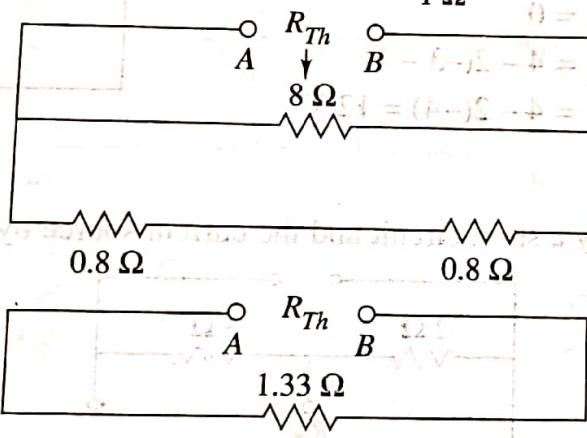
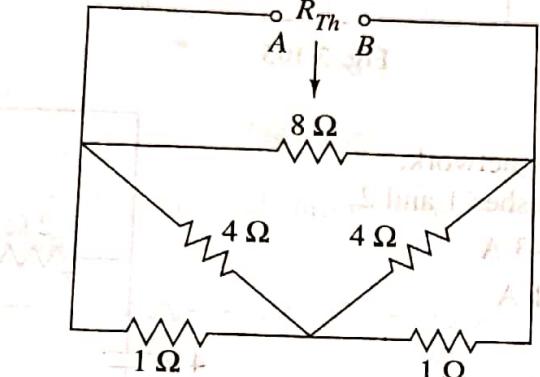


Fig. 3.103

Step III: Calculation of I_L

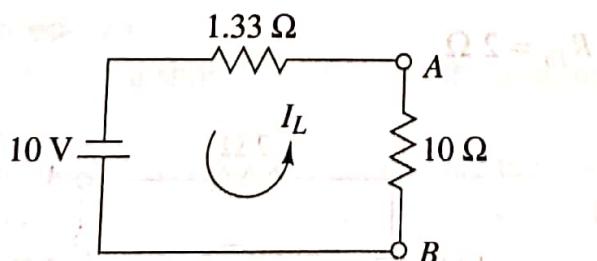


Fig. 3.104

$$I_L = \frac{10}{1.33 + 10} = 0.88\text{ A} (\uparrow)$$

Example 3.23 Find the current through the 1Ω resistor.

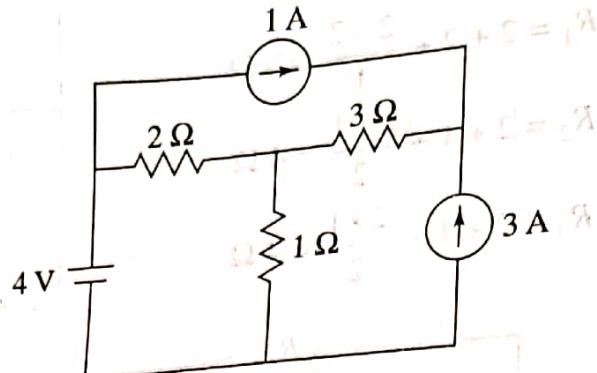


Fig. 3.105

Step I: Calculation of V_{Th}

Removing the 1Ω resistor from the network,
Writing the current equation for Meshes 1 and 2,

$$I_1 = -3 \text{ A}$$

$$I_2 = 1 \text{ A}$$

Writing V_{Th} equation,

$$4 - 2(I_1 - I_2) - V_{Th} = 0$$

$$V_{Th} = 4 - 2(-3 - 1)$$

$$= 4 - 2(-4) = 12 \text{ V}$$

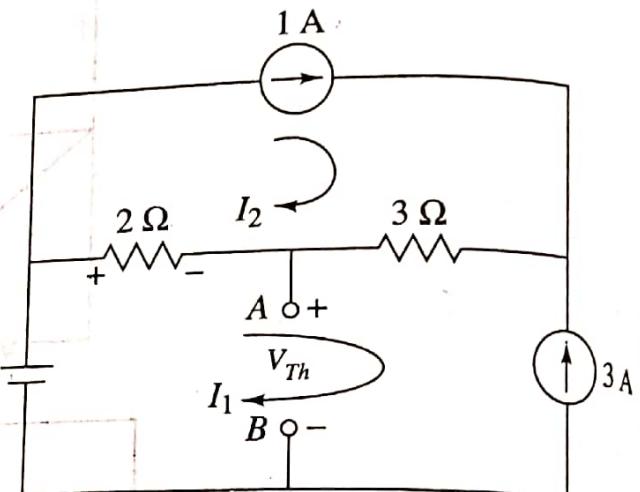


Fig. 3.106

Step II: Calculation of R_{Th}

Replacing the voltage source by a short circuit and the current source by an open circuit,

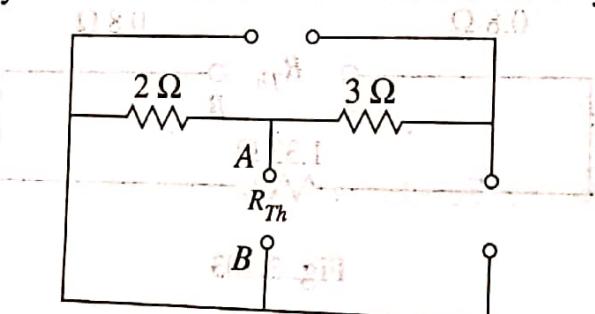


Fig. 3.107

Step III: Calculation of I_L

$$R_{Th} = 2 \Omega$$

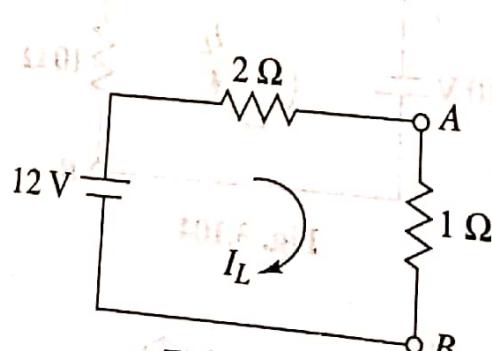


Fig. 3.108


$$I_L = \frac{12}{2+1} = 4 \text{ A}$$

11

Maximum Power Transfer Theorem.

It states that the Maximum power is delivered from a source to a load when the load Resistance is equal to the source resistance.

$$I = \frac{V}{R_s + R_L}$$

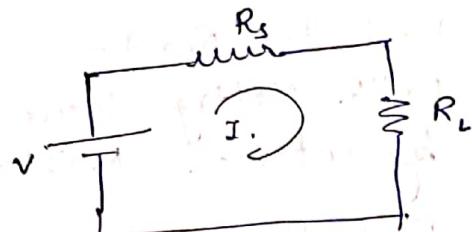

Power delivered to the load

$$R_L \Rightarrow P = I^2 R_L = \frac{V^2 R_L}{(R_s + R_L)^2}$$

→ To determine the value of R_L for max. Power to be transferred to the load.

$$\frac{dP}{dR_L} = 0$$

$$\begin{aligned} \frac{dP}{dR_L} &= \frac{d}{dR_L} \left\{ \frac{V^2}{(R_s + R_L)^2} R_L \right\} \\ &= \frac{V^2 [(R_s + R_L)^2 - 2R_L(R_s + R_L)]}{(R_s + R_L)^4} = 0. \end{aligned}$$

$$(R_s + R_L)^2 - 2R_L(R_s + R_L) = 0.$$

$$R_s^2 + 2R_s R_L + R_L^2 - 2R_L R_s + 2R_L^2 = 0.$$

$$R_s^2 - R_L^2 = 0.$$

$$\boxed{R_s = R_L}.$$


Hence, the max. Power will be transferred to the load resistance is equal to the source resistance.

Steps to be followed. in Maximum Power Transfer Theorem.

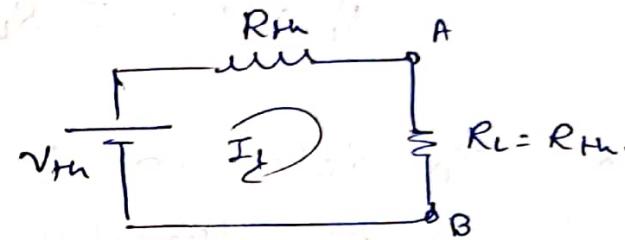- (1) Remove the Variable load resistor ' R_L '.
- (2) Find the open circuit voltage ' V_{th} ' across point A & B.
- (3) Find the Resistance ' R_{th} ' as seen from Point A & B with Voltage source & current source replaced by Internal Resistance.
- (4) Find the resistance R_L for maximum power transfer.
- (5) Find the Max. Power.


$$(R_L = R_{th})$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{V_{th}}{2 R_{th}}$$



$$\begin{aligned} P_{max} &= I_L^2 R_L \\ &= \frac{V_{th}^2}{2 R_{th}} \times R_{th} \Rightarrow P_{max} = \frac{V_{th}^2}{4 R_{th}} \end{aligned}$$

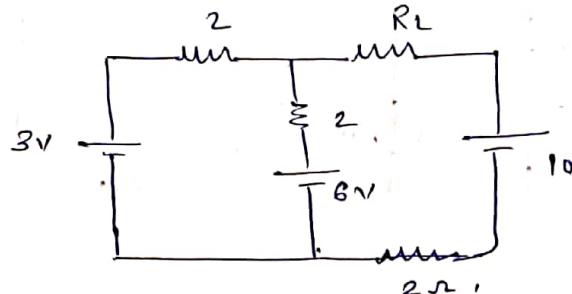Q. Find value of Resistance ' R_L ' for maximum Power & calculate Maximum Power.




$$\Rightarrow V_{th} = ?$$

Remove R_L .

Apply KVL in mesh

$$3 - 2I - 2I - 6 = 0.$$

$$I = -0.75 \text{ Amp}$$

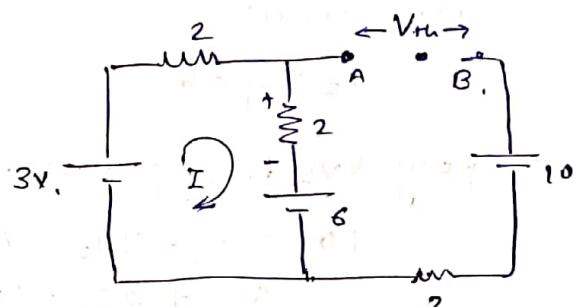

Writing V_{th} eqn.

$$6 + 2I - V_{th} - 10 = 0.$$


$$V_{th} = 6 + 2(-0.75) - 10.$$

$$V_{th} = -5.5 \text{ V.}$$

$V_{th} = 5.5$ (terminal B is positive w.r.t A)

IV) $R_{th} = ?$

$$R_{th} = (2||2) + 2 = 3 \Omega.$$

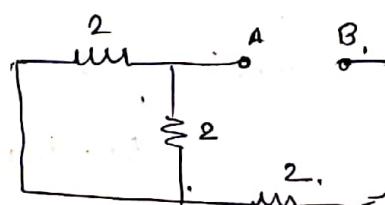

III) Value of R_L .


Max. Power transfer

$$R_L = R_{th} = 3 \Omega.$$


IV) Cal'n of P_{max} .

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{5.5^2}{4 \times 3}$$

$$P_{max} = 2.52 \text{ W.}$$

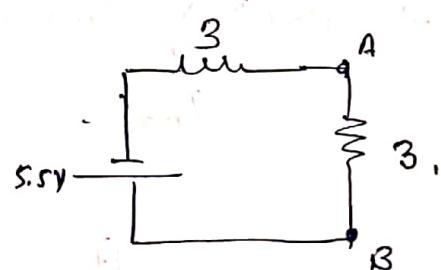

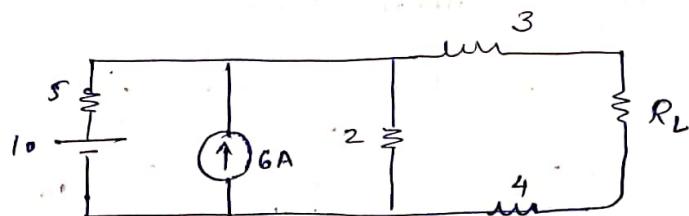Q. Find value of Resistance R_L for max. Power & Calculate max. Power.




\Rightarrow ① $V_{Th} = ?$

Remove R_L from circuit.

From circuit

$$I_2 - I_1 = 6$$

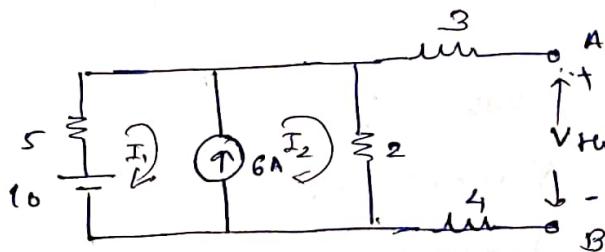

Apply KVL in supernode.

$$10 - 5I_1 - 2I_2 = 0$$

$$5I_1 + 2I_2 = 10$$


$$I_1 = -0.29 \text{ A} ; \quad I_2 = 5.71 \text{ A}$$

Waiting V_{Th} Eq^n;

$$V_{Th} = 2I_2 = 11.42 \text{ V}$$


② $R_{Th} = ?$
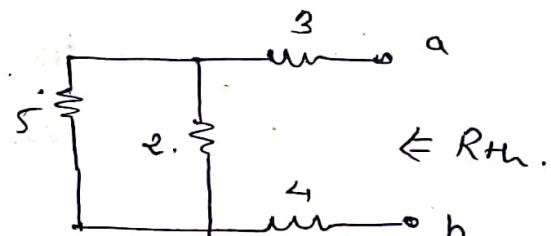
$$R_{Th} = (5//2) + 3 + 4 = 8.43 \Omega$$



③ Cal^n of R_L

$$R_L = R_{Th} = 8.43 \Omega$$

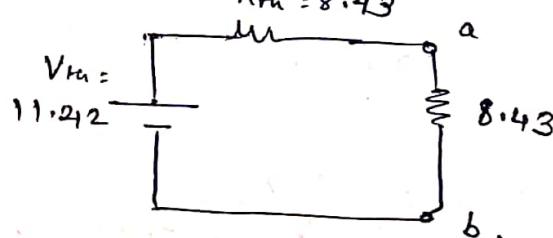


④ Cal^n of P_{max} .

$$P_{max} = \frac{V_{Th}^2}{4 \times R_{Th}} = \frac{(11.42)^2}{4 \times 8.43}$$

$$\boxed{P_{max} = 3.87 \text{ W}}$$

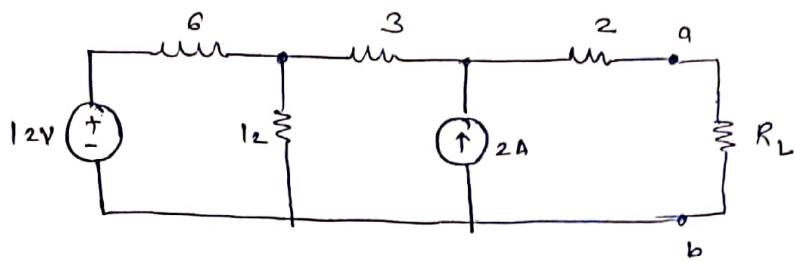
Q. Find the value of R_L for max. Power transfer in the circuit of . Find the max. Power.



$$\Rightarrow \textcircled{1} V_{th} = ?$$

Apply KCL in Node ①.
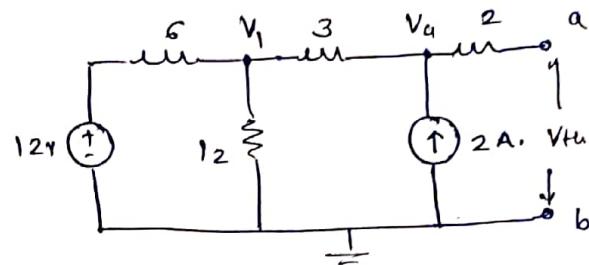
$$\frac{V_1 - 12}{6} + \frac{V_1}{12} + \frac{V_1 - V_a}{3} = 0$$



$$2V_1 - 24 + V_1 + 4V_1 - 4V_a = 0.$$

$$7V_1 - 4V_a = 24 \quad \text{--- (1)}$$

Apply KCL in Node ②.

$$\frac{V_a - V_1}{3} - 2 = 0 \Rightarrow V_a - V_1 = 6 \quad \text{--- (2)}$$


From Eqn ① & ② ; $V_1 = 16V$; $V_a = 22V$.

$$V_a = V_{th} = 22V$$

$$\Rightarrow \textcircled{2} R_{th} = ?$$

$$R_{th} = (6 \parallel 3) + 3 + 2 = 4 + 3 + 2$$


$$\boxed{R_{th} = 9\Omega}$$

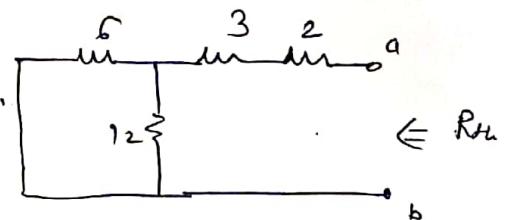

③ Value of R_L

for max Power

$$R_L = R_{th} = 9\Omega$$

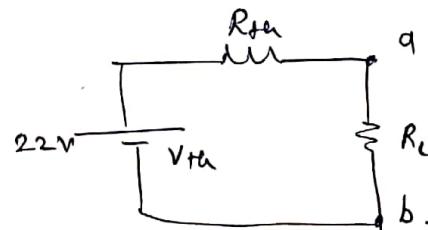

④ Cal'n of P_{max} .

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{22^2}{4 \times 9} = \frac{484}{36}.$$

$$\boxed{P_{max} = 13.44 \text{ Watts}}$$

Example 3.42 For the circuit shown, find the value of the resistance R_L for maximum power and calculate the maximum power.

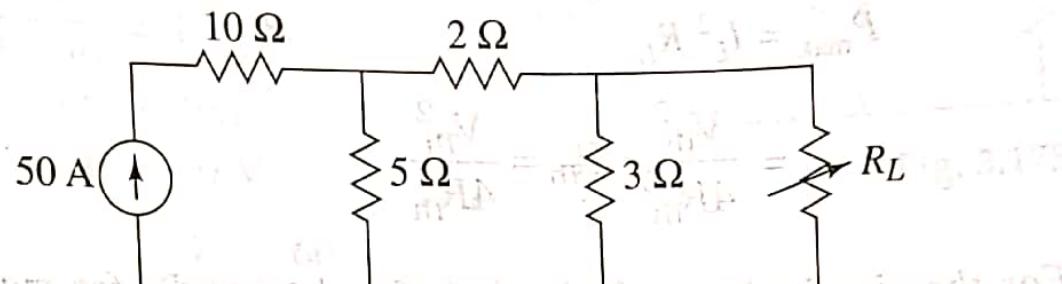


Fig. 3.182

Step I: Calculation of V_{Th}

Removing the variable resistor R_L from the circuit,
For Mesh 1,

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$5I_1 - 10I_2 = 0$$

$$I_1 = 2I_2$$

$$I_2 = 25 \text{ A}$$

$$V_{Th} = 3I_2 = 3(25) = 75 \text{ V}$$

Step II: Calculation of R_{Th}

Replacing the current source of 50 A with an open circuit,

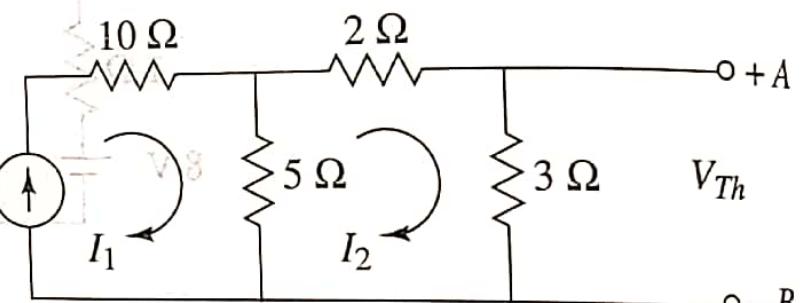


Fig. 3.183

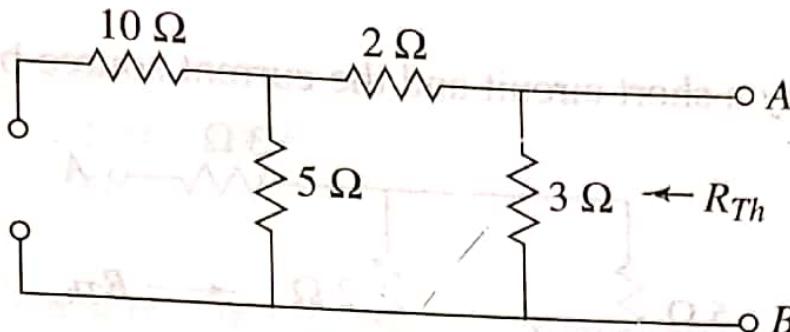


Fig. 3.184

$$R_{Th} = 7 \parallel 3 = 2.1 \Omega$$

Step III: Value of R_L

For maximum power transfer,

$$R_L = R_{Th} = 2.1 \Omega$$

Step IV: Calculation of P_{max}

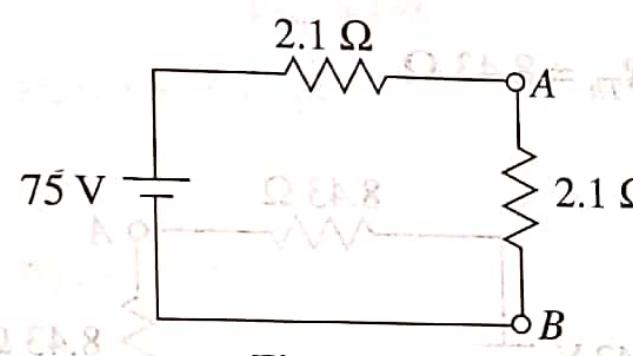


Fig. 3.185

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(75)^2}{4 \times 2.1} = 669.64 \text{ W}$$

Example 3.12

For the circuit shown in Fig. 3.184, calculate the maximum power delivered to the load.

Example 3.44 For the circuit shown, find the value of the resistance R_L for maximum power and calculate the maximum power.

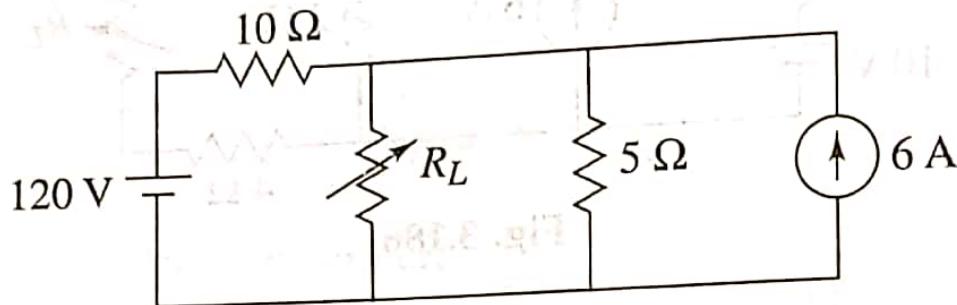


Fig. 3.190

Step I: Calculation of V_{Th}

Removing the variable resistor R_L from the circuit,

Applying KVL to Mesh 1,

$$120 - 10I_1 - 5(I_1 - I_2) = 0 \quad \dots(1)$$

$$15I_1 - 5I_2 = 120$$

Writing current equation for Mesh 2,

$$I_2 = -6 \text{ A} \quad \dots(2)$$

Solving Eqs (1) and (2),

$$I_1 = 6 \text{ A}$$

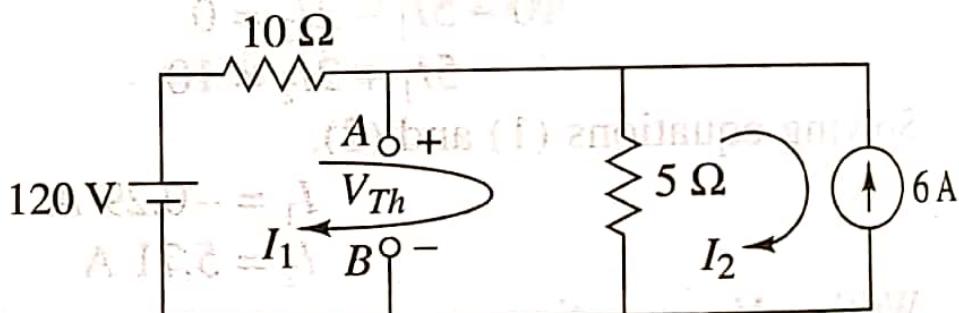


Fig. 3.191

Writing V_{Th} equation,

$$120 - 10I_1 - V_{Th} = 0$$

$$\begin{aligned}V_{Th} &= 120 - 10(6) \\&= 60 \text{ V}\end{aligned}$$

Step II: Calculation of R_{Th}

Replacing the voltage source by a short circuit and the current source by an open circuit,

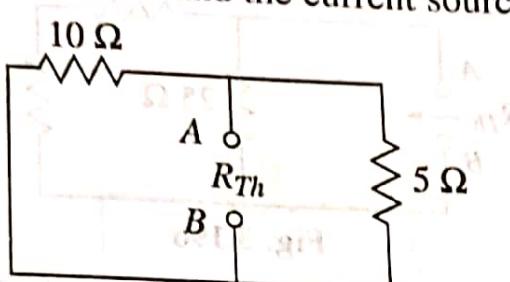


Fig. 3.192

$$R_{Th} = 10 \parallel 5 = 3.33 \Omega$$

Step III: Calculation of R_L

For maximum power transfer

$$R_L = R_{Th} = 3.33 \Omega$$

Step IV: Calculation of P_{max}

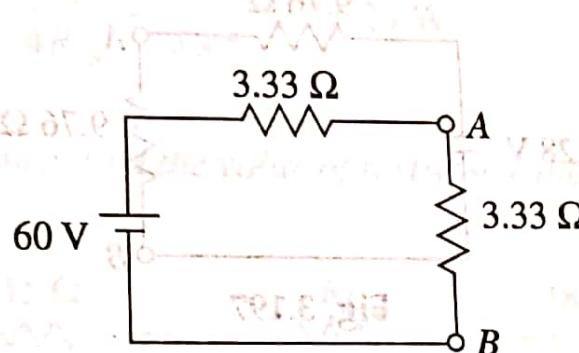


Fig. 3.193

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(60)^2}{4 \times 3.33} = 270.27 \text{ W}$$